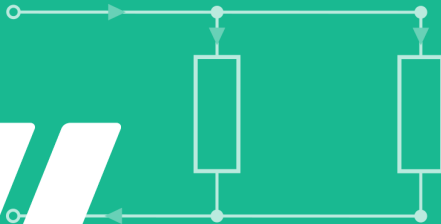


GET it digital

Modul 4: Basic DC networks



Stand: 18. Februar 2026



Further use as OER is expressly permitted: This work and its contents are licensed under CC BY 4.0. Excluded from the license are the logos used as well as all elements marked otherwise. Attribution according to the TULLU rule should be given as follows: “GET it digital module 4: Basic DC networks” by H. Bode, License: CC BY 4.0.

The license agreement is available here:

<https://creativecommons.org/licenses/by/4.0/deed.de>

The work is available online at:

<https://getitdigital.uni-wuppertal.de/module/modul-4-grundlegende-gleichstromnetzwerke>

Electrical networks consist of:


- ▶ Two-pole or multi-pole: Elements with two or more electrical connections
- ▶ Connected by ideal conductive connections

These can be connected to systems of various sizes:

- ▶ Energy distribution networks ≥ 1000 km in length
- ▶ Electronic circuits in the micrometer range (microcontrollers)






Symbolbilder

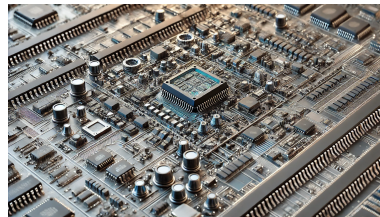

Objective: Calculation of electrical quantities in a circuit

- ▶ Simplification of real components to ideal two-pole circuits
- ▶ Representation of two-pole circuits using equivalent circuit diagrams (see table)
→ form the basis for mathematical calculations
- ▶ Equivalent circuit diagrams model the basic behavior of real electrical circuits

Examples of two poles:

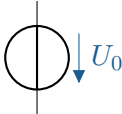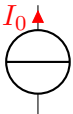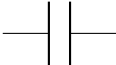Dipole	Circuit symbol
Ideal voltage source	
ideal current source	
Capacitor (capacitance)	
ohmic resistance	
Coil (inductance)	




Learning objectives: Two-terminal elements and reference direction systems

The students can

- ▶ explain the concept of two poles, name common two poles and use their circuit symbols
- ▶ explain the generator and consumer arrow system and apply it in accordance with conventions
- ▶ explain the central elements of the basic circuit and recognise the relationships between them

Generally:

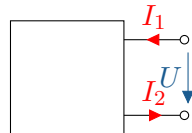- ▶ Two external connections
- ▶ Clamping currents I_1 and I_2 are equal in magnitude ($I_1 = I_2 = I$)
- ▶ Clamping behaviour (ratio of I and U)
- ▶ Actual construction dimensions, material properties, and field strength distribution in the component are neglected.





Active two-phase: contains current/voltage source(s) and, if necessary, resistors, capacitors, coils...

Passive two-pole: Contains no sources, only resistors, capacitors, coils...


Sign convention

Zählfeilrichtung theoretisch beliebig, jedoch Konventionen:

- ▶ Passive sign convention (PSC): Current and voltage **In the same way** (passive two-pole devices, e.g. resistors)
- ▶ Generator sign convention (GSC): Current and voltage **Opposite** (active two-pole devices, e.g. voltage sources)

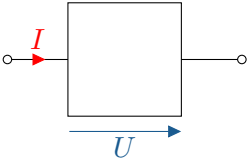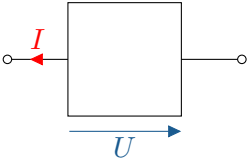sign convention	Generated power	Consumed power	Passive sign-convention arrows
PSC	$P = -UI$	$P = UI > 0$	
ASC	$P = UI > 0$	$P = -UI$	

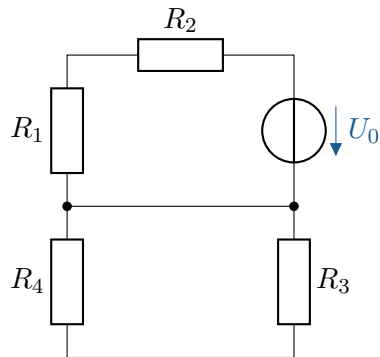
The most important terms are shown in the illustration:



The basic circuit

The most important terms are shown in the illustration:

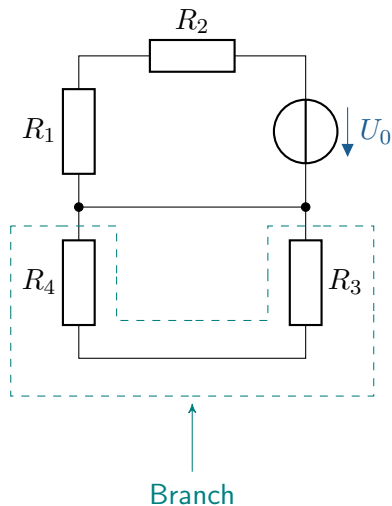
- idealised two-poles form **branches** of the network



The basic circuit

The most important terms are shown in the illustration:

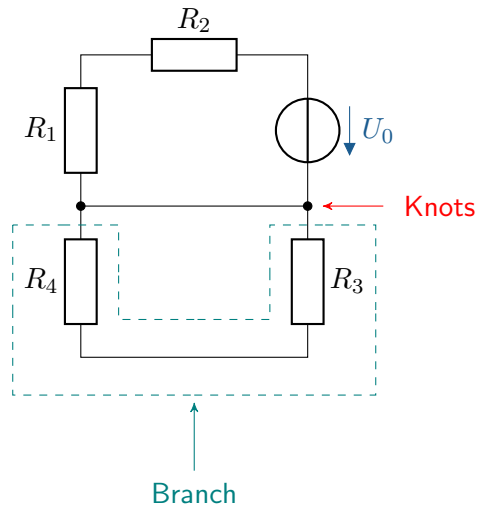
- ▶ idealised two-poles form **branches** of the network
- ▶ Connection of the individual branches via **Knots** K_n



The basic circuit

The most important terms are shown in the illustration:

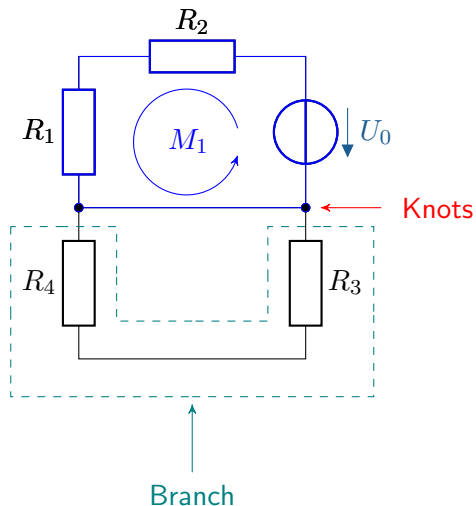
- ▶ idealised two-poles form **branches** of the network
- ▶ Connection of the individual branches via **Knots** K_n
- ▶ Forms a closed chain of branches
Mesh M_n



The basic circuit

The most important terms are shown in the illustration:

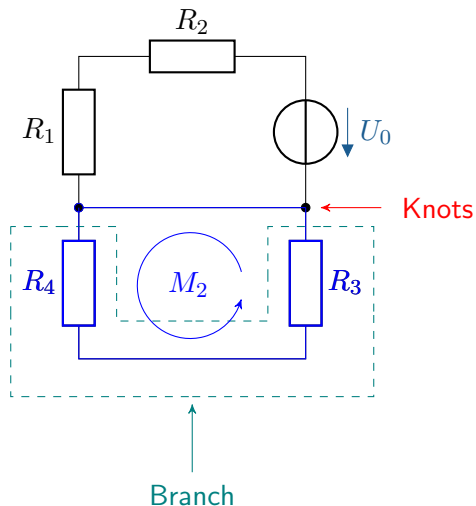
- ▶ idealised two-poles form **branches** of the network
- ▶ Connection of the individual branches via **Knots** K_n
- ▶ Forms a closed chain of branches
Mesh M_n



The basic circuit

The most important terms are shown in the illustration:

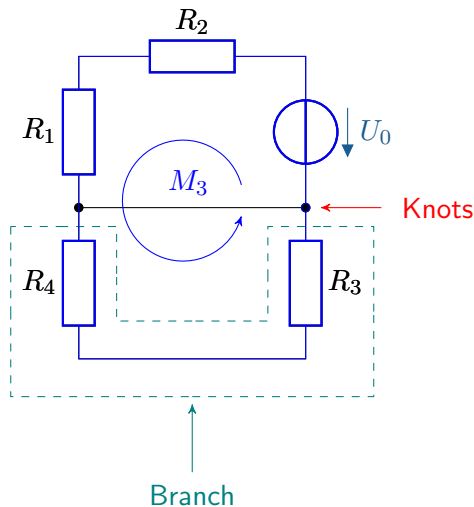- ▶ idealised two-poles form **branches** of the network
- ▶ Connection of the individual branches via **Knots** K_n
- ▶ Forms a closed chain of branches
Mesh M_n




The basic circuit

The most important terms are shown in the illustration:

- ▶ idealised two-poles form **branches** of the network
- ▶ Connection of the individual branches via **Knots** K_n
- ▶ Forms a closed chain of branches
Mesh M_n

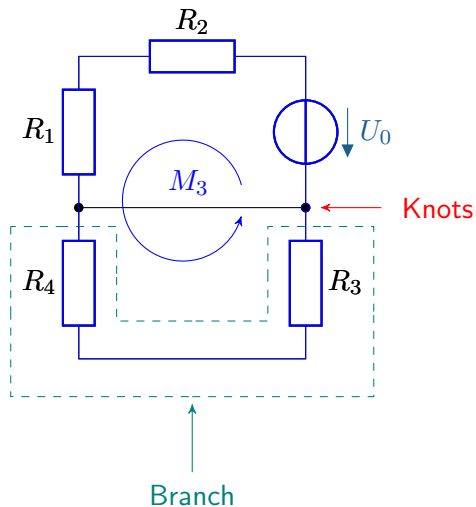How are current and voltage distributed in a network?



Learning objectives: Kirchhoff's rules

The students can


- ▶ reproduce the key statements of Kirchhoff's rules
- ▶ apply Kirchhoff's rules to simple resistance networks

Node rule I (Kirchhoff's 1st law)

Key point:

Total inflows
=
Total outflows
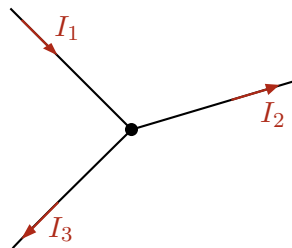
$$\sum I_{\text{in}} = \sum I_{\text{out}}$$



$$I_1 = I_2 + I_3$$

Node rule I (Kirchhoff's 1st law)


Key point:

Total inflows
=
Total outflows

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

Alternatively: count incoming currents as positive and outgoing currents as negative:


$$\sum_{k=1}^n I_k = 0$$

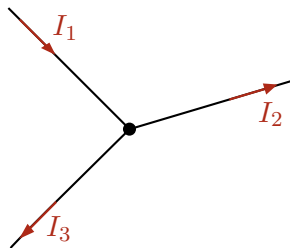

$$I_1 = I_2 + I_3$$


$$I_1 - I_2 - I_3 = 0$$

Application to envelope nodes:

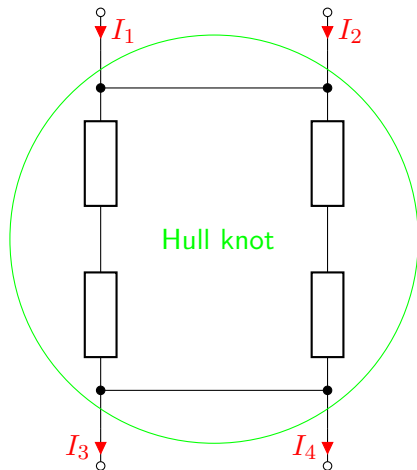


$$I_1 + I_2 - I_3 - I_4 = 0$$

Application to envelope nodes:

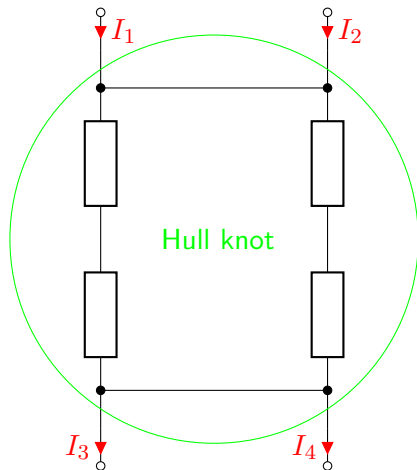

$$I_1 + I_2 - I_3 - I_4 = 0$$


Application to geometric structures:

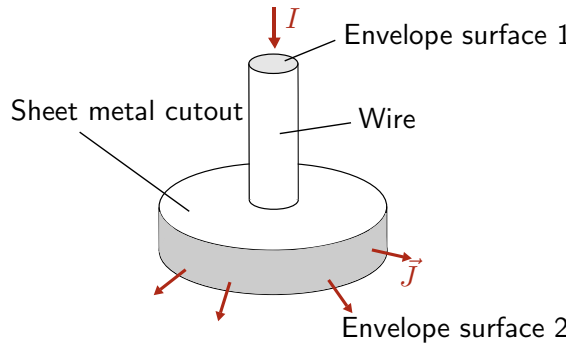

$$\iint_A \vec{J} \cdot d\vec{A} = 0$$

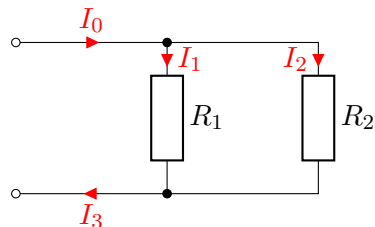Example: Parallel connection of resistors

In a parallel circuit, the currents split at the common node. How large is the current I_3 ?



Example: Parallel connection of resistors


In a parallel circuit, the currents split at the common node. How large is the current I_3 ?

$$I_0 - I_1 - I_2 = 0$$

$$I_0 = I_1 + I_2$$

$$I_1 + I_2 = I_3$$

$$\rightarrow I_3 = I_0$$

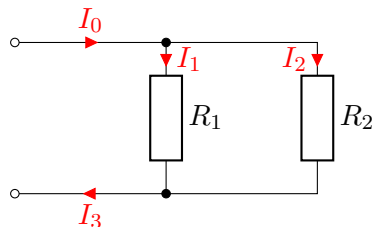

Example: Parallel connection of resistors

In a parallel circuit, the currents split at the common node. How large is the current I_3 ?



$$I_0 - I_1 - I_2 = 0$$

$$I_0 = I_1 + I_2$$

$$I_1 + I_2 = I_3$$

$$\rightarrow I_3 = I_0$$

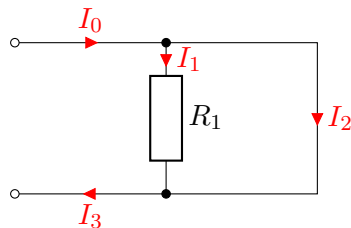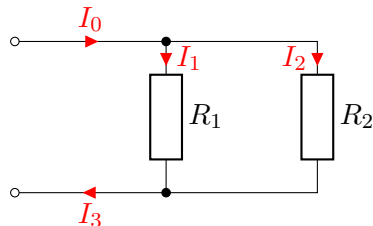A resistor is replaced by a conductive connection.
How strong is the current? I_2 ?



Example: Parallel connection of resistors

In a parallel circuit, the currents split at the common node. How large is the current I_3 ?

$$I_0 - I_1 - I_2 = 0$$

$$I_0 = I_1 + I_2$$

$$I_1 + I_2 = I_3$$

$$\rightarrow I_3 = I_0$$

A resistor is replaced by a conductive connection.
How strong is the current? I_2 ?



$$I_0 = I_1 + I_2$$

$$U_2 = R_2 \cdot I_2 = 0 \cdot I_2$$

$$U_1 = R_1 \cdot I_1 \stackrel{!}{=} U_2 = 0$$

$$\rightarrow I_1 = 0$$

$$\rightarrow I_2 = I_0 = I_3$$

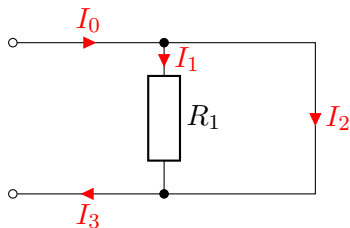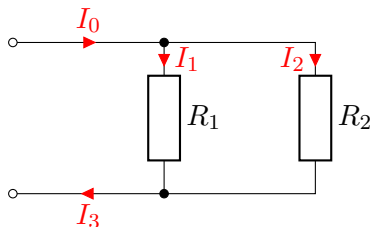


Mesh rule (Kirchhoff's second law)

With closed mesh circulation:

Key point:

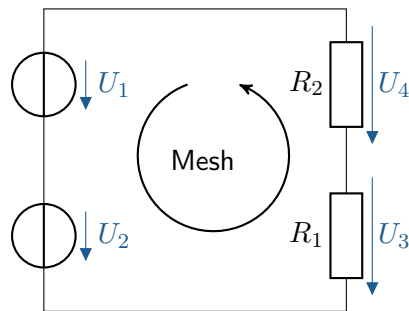Sum of voltage sources
=
Total voltage at consumers



$$U_1 + U_2 = U_3 + U_4$$

Mesh rule (Kirchhoff's second law)

With closed mesh circulation:

Key point:


Sum of voltage sources
=
Total voltage at consumers

Or:

With the mesh circulation closed, add up the partial stresses with the correct sign.

Merke:

$$\sum_{k=1}^n U_k = 0$$

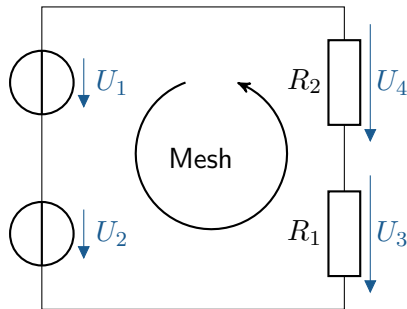

$$U_1 + U_2 = U_3 + U_4$$

$$U_1 + U_2 - U_3 - U_4 = 0$$

Mesh rule (Kirchhoff's second law)

With closed mesh circulation:

Key point:


Sum of voltage sources
=
Total voltage at consumers

Or:

With the mesh circulation closed, add up the partial stresses with the correct sign.

Merke:

$$\sum_{k=1}^n U_k = 0$$

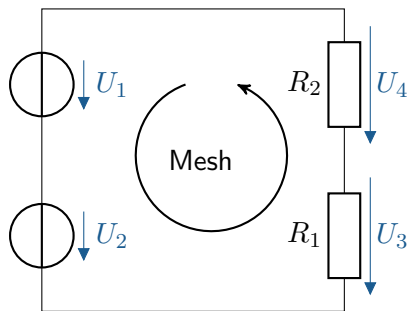

$$U_1 + U_2 = U_3 + U_4$$

$$U_1 + U_2 - U_3 - U_4 = 0$$


General description according to Maxwell's equations:

$$\oint_s \vec{E} d\vec{s} = 0$$

Example: Series connection of resistors

In a series connection, the voltages add up to a total voltage.

How high is the voltage? U_0 ?

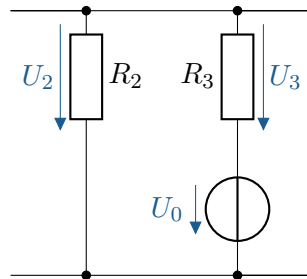


Example: Series connection of resistors

In a series connection, the voltages add up to a total voltage.

How high is the voltage? U_0 ?

$$U_2 - U_0 - U_3 = 0$$

$$\rightarrow U_0 = U_2 - U_3$$

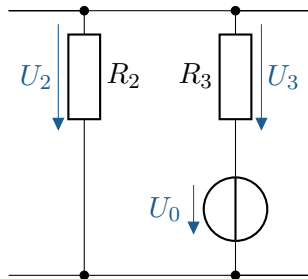

Example: Series connection of resistors



In a series connection, the voltages add up to a total voltage.

How high is the voltage? U_0 ?

$$U_2 - U_0 - U_3 = 0$$

$$\rightarrow U_0 = U_2 - U_3$$

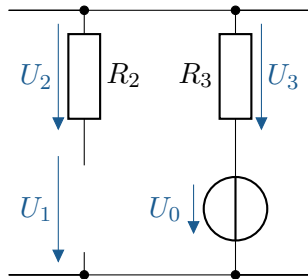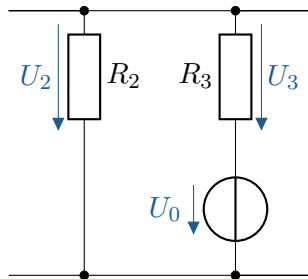A connection is interrupted. How large is the voltage U_1 at the point of interruption?



Example: Series connection of resistors

In a series connection, the voltages add up to a total voltage.

How high is the voltage? U_0 ?

$$U_2 - U_0 - U_3 = 0$$

$$\rightarrow U_0 = U_2 - U_3$$

A connection is interrupted. How large is the voltage U_1 at the point of interruption?



$$U_2 + U_1 - U_0 - U_3 = 0$$

$$U_2 = I_2 \cdot R_2$$

$$\rightarrow I_2 = 0$$

$$\rightarrow U_2 = 0$$

$$U_1 = U_0 + U_3$$

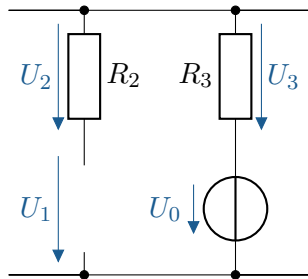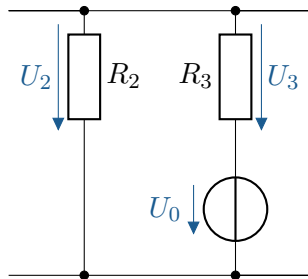

Learning objectives: Simple resistance networks

The students can

- ▶ Identify subcircuits in direct current networks
- ▶ Simplify and summarise resistance networks
- ▶ Determine short-circuit and no-load data
- ▶ Apply superposition methods



Series connection of resistors

Mesh rule:

$$U_0 - U_1 - U_2 = 0$$

Ohm's law:
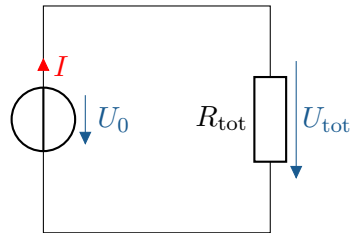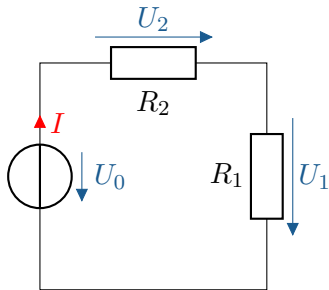
$$U_1 = R_1 \cdot I \quad U_2 = R_2 \cdot I$$



$$U_0 - R_{\text{tot}} \cdot I = 0$$

$$R_{\text{tot}} = R_1 + R_2$$

Series connection of resistors

Mesh rule:

$$U_0 - U_1 - U_2 = 0$$

Ohm's law:



$$U_1 = R_1 \cdot I \quad U_2 = R_2 \cdot I$$

The current I flows through all components:

$$U_0 - R_1 \cdot I - R_2 \cdot I = 0$$

$$U_0 - (R_1 + R_2) \cdot I = 0$$

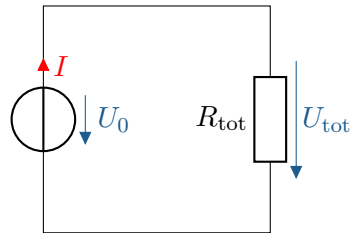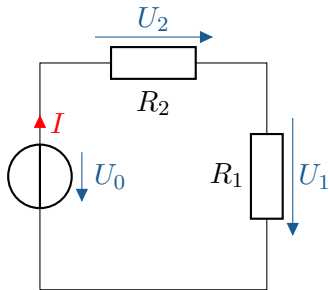Total resistance of a series connection of resistors:



$$U_0 - R_{\text{tot}} \cdot I = 0$$

$$R_{\text{tot}} = R_1 + R_2$$

Key point:

$$R_{\text{tot}} = \sum_{k=1}^n R_k$$

Series connection of resistors

Mesh rule:

$$U_0 - U_1 - U_2 = 0$$

Ohm's law:



$$U_1 = R_1 \cdot I \quad U_2 = R_2 \cdot I$$

The current I flows through all components:

$$U_0 - R_1 \cdot I - R_2 \cdot I = 0$$

$$U_0 - (R_1 + R_2) \cdot I = 0$$

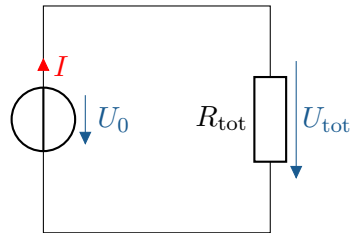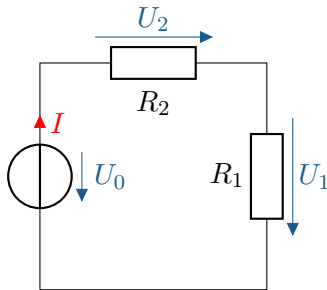Total resistance of a series connection of resistors:



$$U_0 - R_{\text{tot}} \cdot I = 0$$

$$R_{\text{tot}} = R_1 + R_2$$

Total conductance of a series connection of resistors:

Key point:

$$R_{\text{tot}} = \sum_{k=1}^n R_k$$

Key point:

$$\frac{1}{G_{\text{tot}}} = \sum_{k=1}^n \frac{1}{G_k}$$

Parallel connection of resistors


Mesh rule: $U_{R1} = U_{R2} = U_0$

Knot rule: $I_0 - I_1 - I_2 = 0$

Ohm's law: $I_1 = \frac{U_0}{R_1}$

$$I_0 - \frac{U_0}{R_1} - \frac{U_0}{R_2} = 0$$
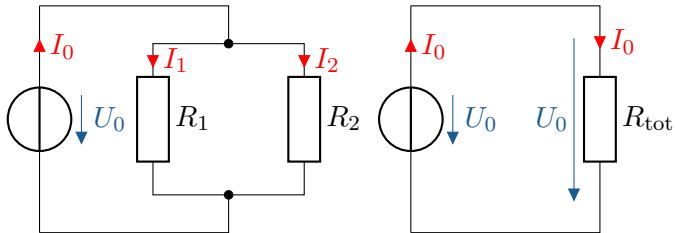
$$I_0 - \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot U_0 = 0$$



Key point:

$$G_{tot} = \sum_{k=1}^n G_k$$

Parallel connection of resistors


Mesh rule: $U_{R1} = U_{R2} = U_0$

Knot rule: $I_0 - I_1 - I_2 = 0$

Ohm's law: $I_1 = \frac{U_0}{R_1}$

$$I_0 - \frac{U_0}{R_1} - \frac{U_0}{R_2} = 0$$
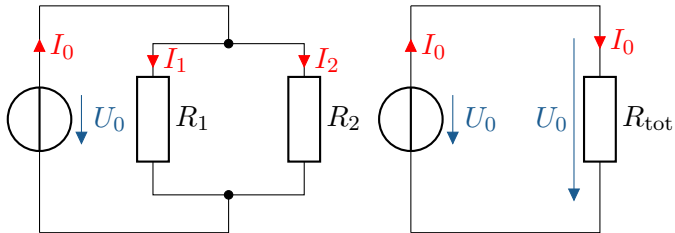
$$I_0 - \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot U_0 = 0$$



Key point:

$$\frac{1}{R_{\text{tot}}} = \sum_{k=1}^n \frac{1}{R_k}$$

Key point:

$$G_{\text{tot}} = \sum_{k=1}^n G_k$$

Voltage dividers in resistor networks

Series connection divides voltage U_0 ,
Current identical in all components


$$I = \frac{U_1}{R_1} = \frac{U_2}{R_2}$$

Series connection of resistors:

$$I = \frac{U_0}{R_1 + R_2}$$

Relationship between total voltage U_0
and partial voltage U_2 :
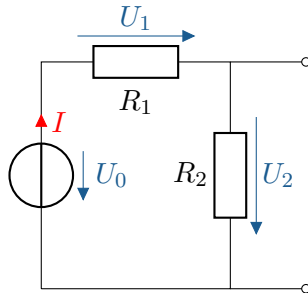
$$\frac{U_2}{R_2} = \frac{U_0}{R_1 + R_2}$$



Key point:

$$U_2 = U_0 \cdot \frac{R_2}{R_1 + R_2}$$

Voltage dividers in resistor networks

Series connection divides voltage U_0 ,
Current identical in all components


$$I = \frac{U_1}{R_1} = \frac{U_2}{R_2}$$

Series connection of resistors:

$$I = \frac{U_0}{R_1 + R_2}$$

Relationship between total voltage U_0
and partial voltage U_2 :
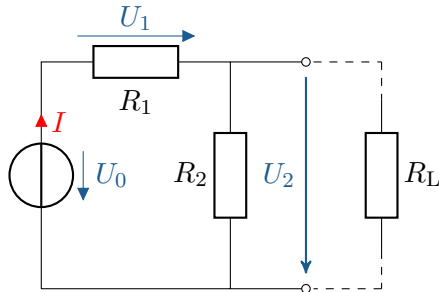
$$\frac{U_2}{R_2} = \frac{U_0}{R_1 + R_2}$$



Key point:

$$U_2 = U_0 \cdot \frac{R_2}{R_1 + R_2}$$

Only applies to **unloaded voltage dividers**
(load current = 0)!

Load case: Combine R_2 and R_L !

Current dividers in resistor networks

Parallel connection divides current I_0 ,
voltage identical across all components


$$U_0 = I_1 \cdot R_1 = I_2 \cdot R_2$$

Parallel connection of resistors:

$$U_0 = I_0 \cdot R_{\text{tot}}$$

$$I_2 \cdot R_2 = I_0 \cdot R_{\text{tot}}$$
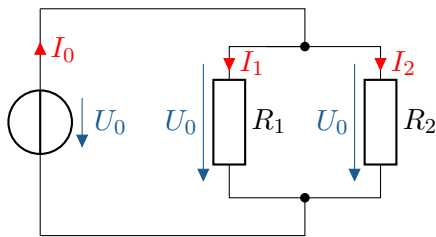
$$I_2 \cdot R_2 = I_0 \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$



$$R_{\text{tot}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

Key point:

$$I_2 = I_0 \cdot \frac{R_1}{R_1 + R_2}$$


The real source of tension

Possesses internal resistance R_i

Unloaded real voltage source:

$$I = 0 \rightarrow U_{Ri} = 0$$

$$U = U_0$$

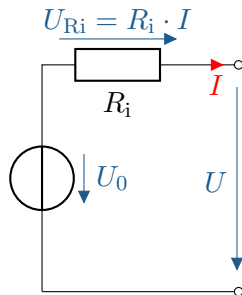

The real source of tension

Possesses internal resistance R_i

Unloaded real voltage source:

$$I = 0 \rightarrow U_{Ri} = 0$$

$$U = U_0$$


Loaded real voltage source:

$$I > 0 \rightarrow U_{Ri} > 0$$

$$U = U_0 - U_{Ri} < U_0$$

Internal resistance as low as possible:

$$U_0 \gg I \cdot R_i$$

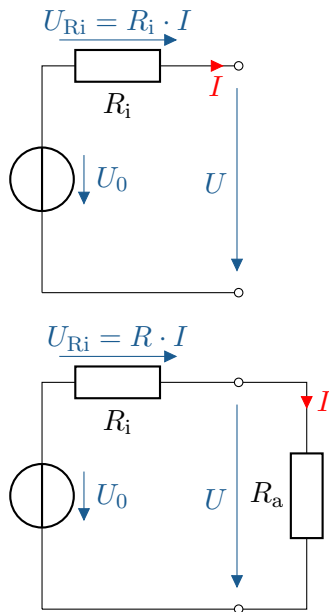


The replacement voltage source

Each **active** two-pole can be represented as a **substitute voltage source**

Ideal voltage source U_0 and **Internal resistance** R_i

$$U_0 = U_{R_i} + U$$

$$U_0 = I \cdot R_i + U$$

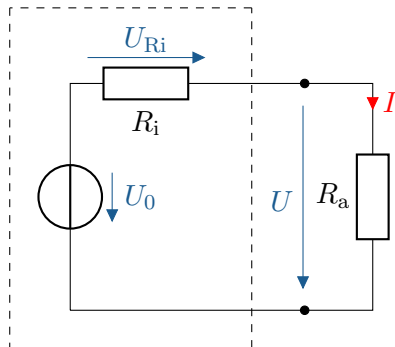

The replacement voltage source

Each **active** two-pole can be represented as a **substitute voltage source**



Ideal voltage source U_0 and **Internal resistance** R_i

$$U_0 = U_{Ri} + U$$

$$U_0 = I \cdot R_i + U$$

Reduction of voltage at the output:

$$U = U_0 - I \cdot R_i$$

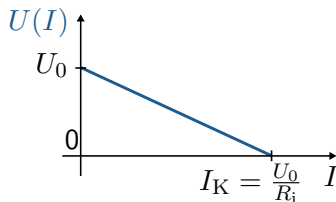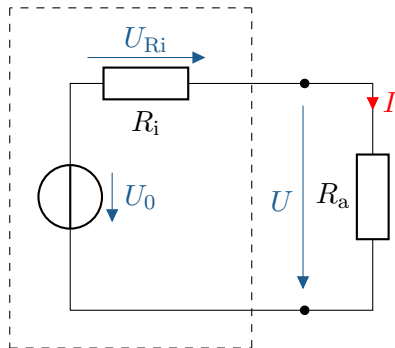



Special operating conditions of the backup voltage source

Determination of U_0 and R_i via **short circuit** and **no-load test**:

Short circuit: $R_a = 0$, $I = I_K$ = short-circuit current

$$U = 0 \rightarrow U_0 = U_{Ri}$$
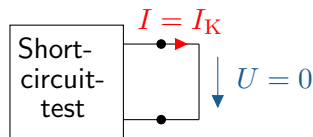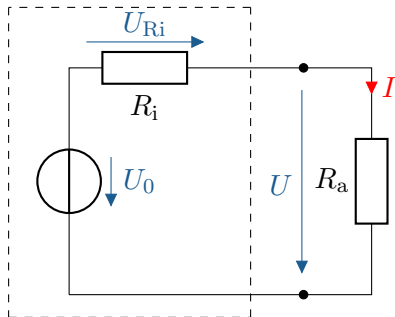
$$U_{Ri} = R_i \cdot I_K \rightarrow I_K = \frac{U_0}{R_i}$$



Special operating conditions of the backup voltage source

Determination of U_0 and R_i via **short circuit** and **no-load test**:

Short circuit: $R_a = 0$, $I = I_K$ = short-circuit current

$$U = 0 \rightarrow U_0 = U_{Ri}$$




$$U_{Ri} = R_i \cdot I_K \rightarrow I_K = \frac{U_0}{R_i}$$

No load: $R_a \rightarrow \infty$, $U = U_L$ = no-load voltage

$$I = 0 \rightarrow U_{Ri} = R_i \cdot 0 = 0$$
$$U_L = U_0$$

Key point:
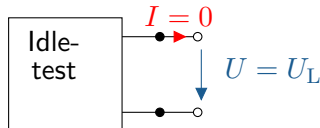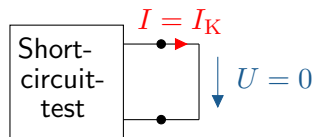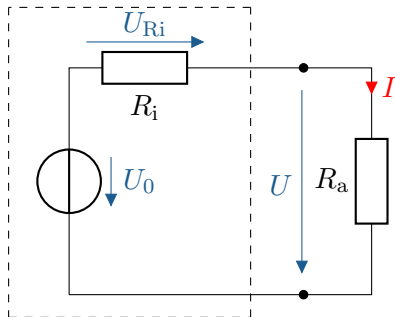
$$U_0 = U_L, \quad R_i = \frac{U_L}{I_K}$$




The real current source

Ideale Current source:
Internal resistance infinite:

$$I_{R_i} = 0$$

$$I = I_0$$

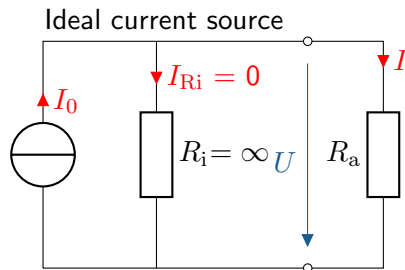


The real current source

Ideale Current source:

Internal resistance infinite:

$$I_{Ri} = 0$$

$$I = I_0$$

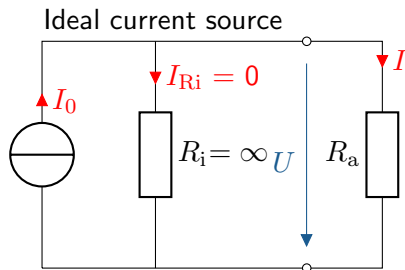

Reale Current source:


Possesses internal resistance $R_i < \infty \Omega$

$$I_{Ri} > 0$$

$$I = I_0 - I_{Ri} < I_0$$

Internal resistance as high as possible:

$$I_0 \gg U/R_i$$

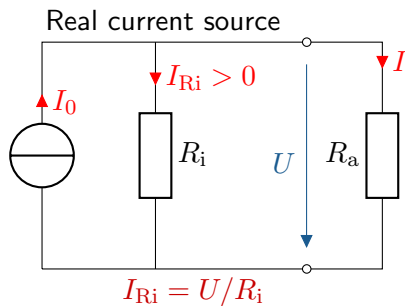

The backup current source

Each **active** two-pole can be represented as a **replacement current source**



Ideal current source I_0 with **internal resistance** R_i

$$I_0 = I_{Ri} + I$$

$$I_0 = \frac{U}{R_i} + I$$

Reduction of output current depending on U :

$$I = I_0 - \frac{U}{R_i}$$

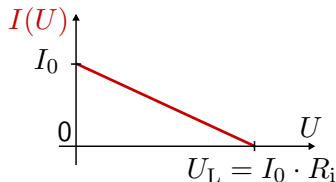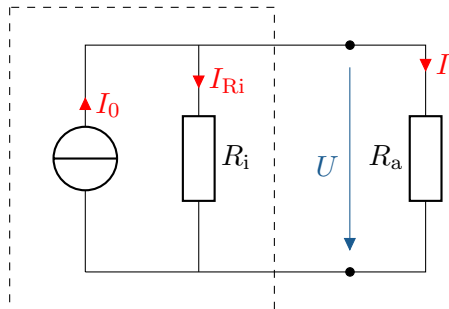



Special operating conditions of the backup power source

Determination of I_0 and R_i via **short circuit** and **no-load test**:

Short circuit: $R_a = 0$, $I = I_K$ = short-circuit current

$$U = 0 \rightarrow I_{Ri} = 0$$

$$I_K = I_0$$

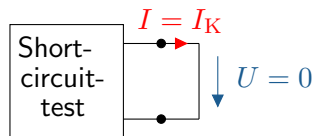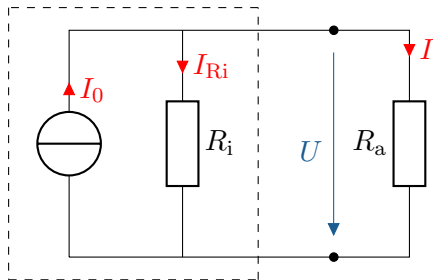

Special operating conditions of the backup power source

Determination of I_0 and R_i via **short circuit** and **no-load test**:

Short circuit: $R_a = 0$, $I = I_K$ = short-circuit current

$$U = 0 \rightarrow I_{Ri} = 0$$

$$I_K = I_0$$




Idling: $R_a \rightarrow \infty$, $U = U_L$ = Open-circuit voltage

$$I = 0 \rightarrow I_{Ri} = I_0$$

$$U_L = R_i \cdot I_0$$

Key point:
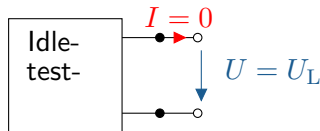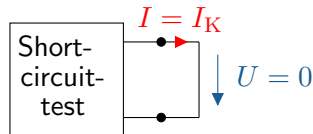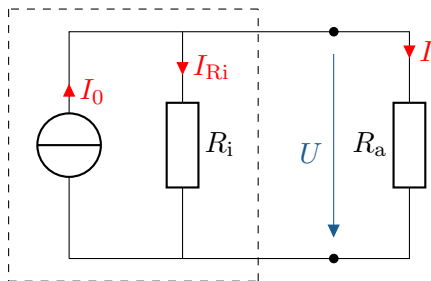
$$I_0 = I_K, \quad R_i = \frac{U_L}{I_K}$$



Conversion of voltage and current sources

Internal resistance R_i remains identical,
Circuit changes

Convert **open-circuit voltage** and **short-circuit current** to another source:


Current source in voltage source:

$$U_0 = I_0 \cdot R_i$$

Voltage source in current source:

$$I_0 = \frac{U_0}{R_i}$$

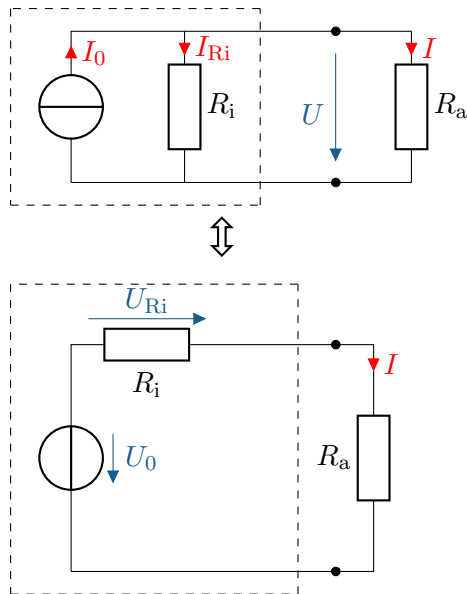The sign Conventions of the sources point in opposite directions!




Parallel connection of capacities

Parallel connection: Voltage of all capacitances identical:

$$U_0 = U_1 = U_2$$

Charge per capacitor:
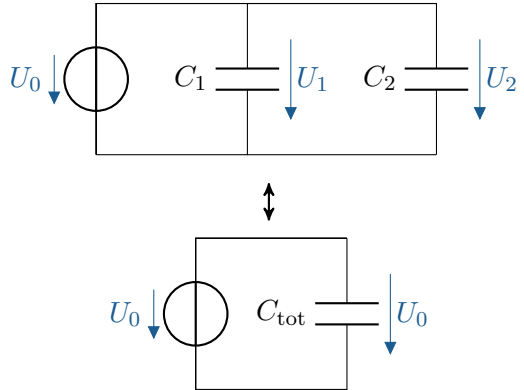
$$Q_k = C_k \cdot U_k, \quad Q_{\text{ges}} = C_{\text{ges}} \cdot U_0$$



Parallel connection of capacities

Parallel connection: Voltage of all capacitances identical:

$$U_0 = U_1 = U_2$$

Charge per capacitor:


$$Q_k = C_k \cdot U_k, \quad Q_{\text{ges}} = C_{\text{ges}} \cdot U_0$$

Total load Q_{ges} :

$$Q_{\text{ges}} = Q_1 + Q_2 = C_1 \cdot U_0 + C_2 \cdot U_0$$

$$Q_{\text{ges}} = (C_1 + C_2) \cdot U_0$$
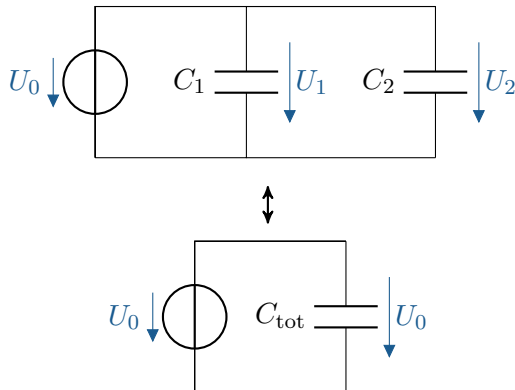
$$\rightarrow C_1 + C_2 = C_{\text{ges}}$$



Key point:

$$C_{\text{tot}} = \sum_{k=1}^n C_k$$

Series connection of capacitances

Series connection: all capacitors have the **same charge Q** !

Basic capacitor equation:

$$Q = C \cdot U$$


$$U_1 = \frac{Q}{C_1}, \quad U_2 = \frac{Q}{C_2}$$

Series connection of capacitances:

$$U_0 = U_1 + U_2 = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \cdot Q$$

Equivalent circuit diagram:
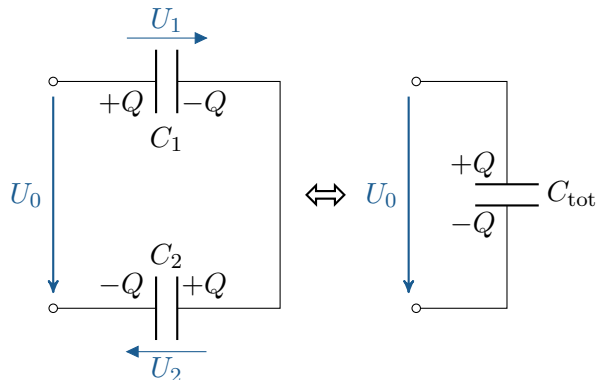
$$U_0 = \frac{1}{C_{\text{tot}}} \cdot Q$$



Key point:

$$\frac{1}{C_{\text{tot}}} = \sum_{k=1}^n \frac{1}{C_k}$$

Voltage divider on capacitances


$$Q_1 = Q_2 = Q_{\text{tot}} = Q$$

$$C_{\text{tot}} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$U_0 = \frac{1}{C_{\text{tot}}} \cdot Q \rightarrow Q = C_{\text{tot}} \cdot U_0$$

$$U_1 = \frac{Q}{C_1} \rightarrow U_1 = \frac{C_{\text{tot}}}{C_1} \cdot U_0$$
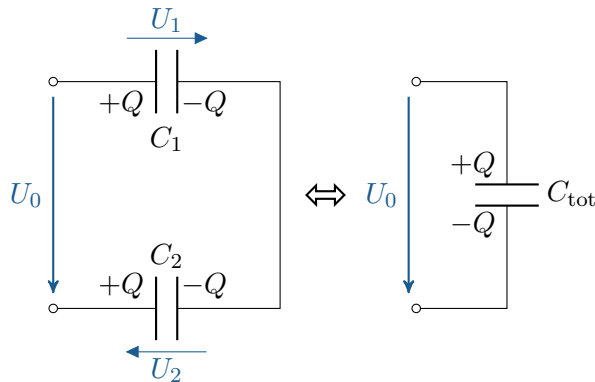
$$U_2 = \frac{Q}{C_2} \rightarrow U_2 = \frac{C_{\text{tot}}}{C_2} \cdot U_0$$




Key point:

$$U_1 = \frac{C_2}{C_1 + C_2} \cdot U_0, \quad U_2 = \frac{C_1}{C_1 + C_2} \cdot U_0$$

Voltage measurement in a direct current circuit

Voltage measurement in a direct current circuit:

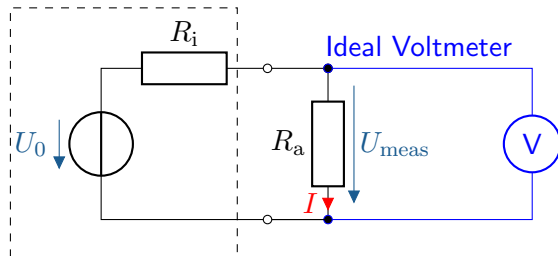- ▶ Measurement with a **voltmeter**
- ▶ Measuring device **parallel** to the component (no interruption of the circuit necessary)




Voltage measurement in a direct current circuit

Voltage measurement in a direct current circuit:

- ▶ Measurement with a **voltmeter**
- ▶ Measuring device **parallel** to the component (no interruption of the circuit necessary)
- ▶ Real voltmeter: **Internal resistance**
 $R_{iV} \gg R_{mess}$
- ▶ measured voltage corrected for internal resistance U_{korr} :


$$U_{\text{korr}} = U \cdot \left(1 + \frac{R_i || R_a}{R_{iV}} \right)$$

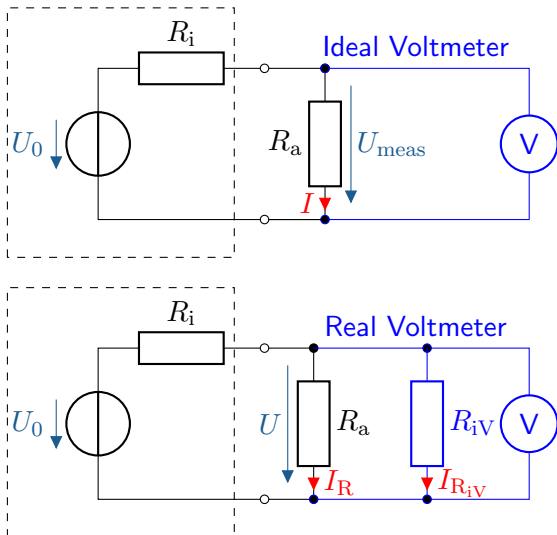

Current measurement in a direct current circuit

Current measurement in a direct current circuit:

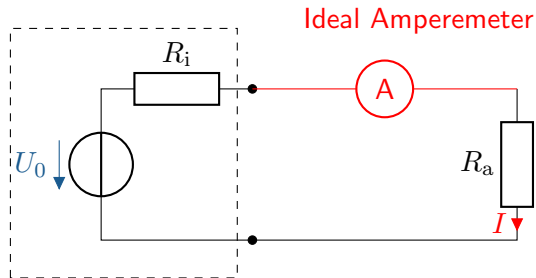- ▶ Measurement with **ammeter**
- ▶ Measuring device **in series** with the component (disconnect the circuit!)




Current measurement in a direct current circuit

Current measurement in a direct current circuit:

- ▶ Measurement with **ammeter**
- ▶ Measuring device **in series** with the component (disconnect the circuit!)
- ▶ Real ammeter: Internal resistance $R_{iA} \ll R_a$
- ▶ Measured current I_{corr} corrected for internal resistance R_{iA} :
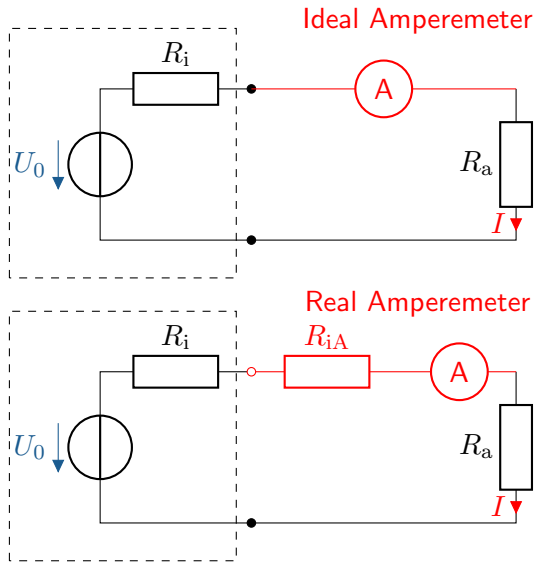
$$I_{\text{corr}} = I \cdot \left(1 + \frac{R_{iA}}{R_i + R_a} \right)$$



Correct measurement of current and voltage I


When measuring current and voltage **simultaneously**:

- ▶ mutual **influence** of the internal resistances **of the measuring instruments**

Current-correct Measurement:

- ▶ greater focus on current strength
- ▶ $U_{\text{meas}} = U_{R_a} + U_{\text{Amperemeter}}$
- ▶ use when the following applies:

$$R_{iA} \ll R_a$$

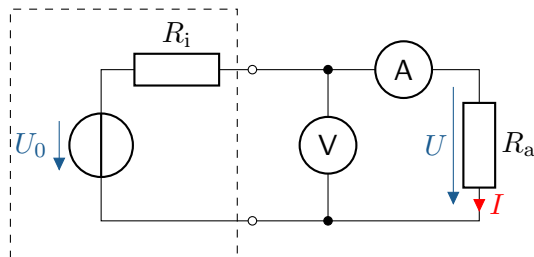

Correct measurement of current and voltage II

Correct voltage measurement:

- ▶ Greater focus on excitement
- ▶ $I_{\text{meas}} = I_{R_a} + I_{\text{Voltmeter}}$
- ▶ Use when applicable:

$$R_{iV} \gg R_a$$

In unclear circumstances:

- ▶ correct current measurement for $R_a > \sqrt{R_{iA} \cdot R_{iV}}$
- ▶ correct voltage measurement for $R_a < \sqrt{R_{iA} \cdot R_{iV}}$

