

GET it digital

Modul 12: Shifting operations



Stand: 18. Februar 2026



Further use as OER is expressly permitted: This work and its contents are licensed under CC BY 4.0. Excluded from the license are the logos used as well as all elements marked otherwise. Attribution according to the TULLU rule should be given as follows: “GET it digital module 12: Shifting operations” by M. Werle, T. Bache, R. Bechler, T. Wever, License: CC BY 4.0.

The license agreement is available here:

<https://creativecommons.org/licenses/by/4.0/deed.de>

The work is available online at:

<https://getitdigital.uni-wuppertal.de/module/modul-12-schaltvorgaenge>



k

Learning objectives: Introduction

The students learn:



- ▶ Recognise switching operations as non-stationary states following switching actions
- ▶ Understand switching operations in the context of other compensation processes
- ▶ Recognise challenges and opportunities associated with switching operations
- ▶ Distinguish between the switching behaviour of ideal and real switches

Settlement procedures

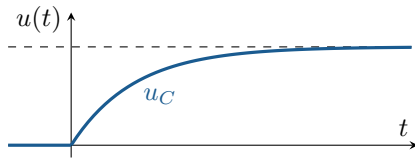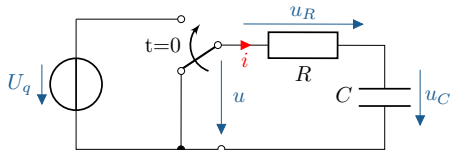

¹Image: Bartolomeo Pinelli, detail from *A Peasant Family Cooking over a Campfire*, Licence CC0 1.0
<https://commons.wikimedia.org/w/index.php?curid=81414513>

Settlement procedures

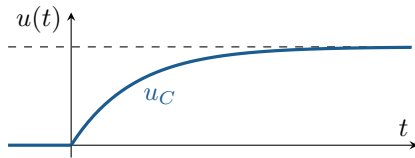
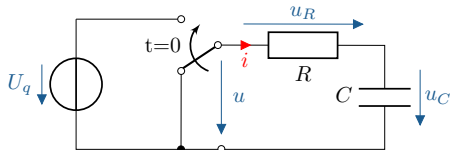


Analogy: Heating water¹



¹Image: Bartolomeo Pinelli, detail from *A Peasant Family Cooking over a Campfire*, Licence CC0 1.0
<https://commons.wikimedia.org/w/index.php?curid=81414513>

Settlement procedures

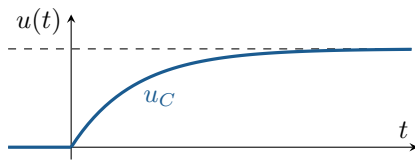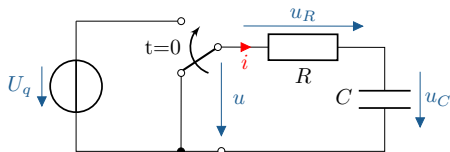

Analogy: Heating water¹






Reasons for balancing transactions:

- ▶ Switching operations
- ▶ DC: Change in voltage/current
- ▶ AC: Change in frequency/amplitude/phase


¹Image: Bartolomeo Pinelli, detail from *A Peasant Family Cooking over a Campfire*, Licence CC0 1.0
<https://commons.wikimedia.org/w/index.php?curid=81414513>

Settlement procedures - Examples

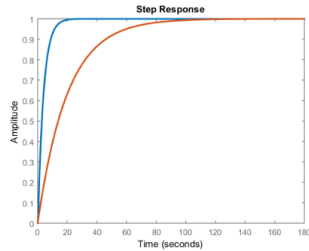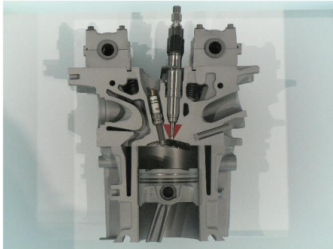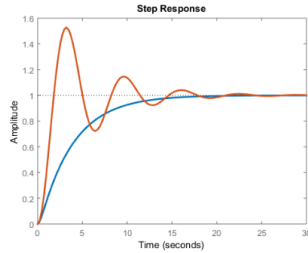


Switching operations

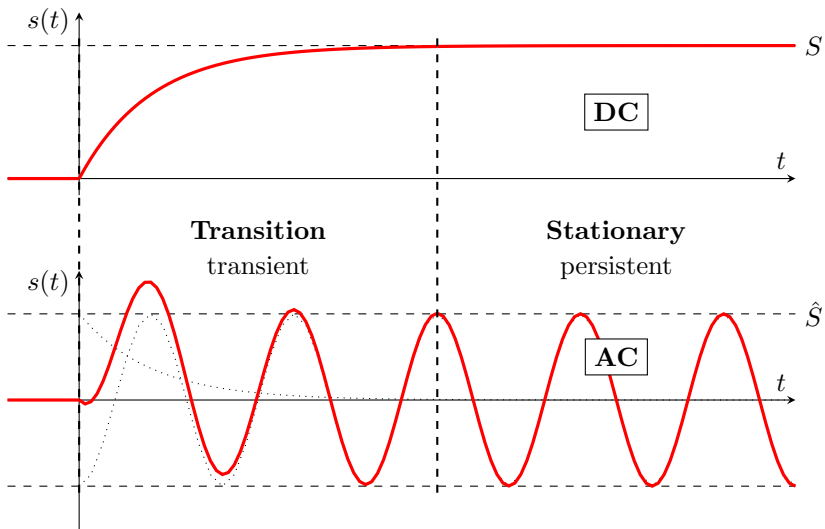Example of switching operation with DC and AC voltage.




Examples of switching operations

Example from power electronics:

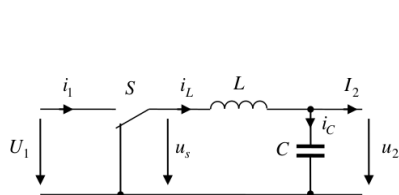

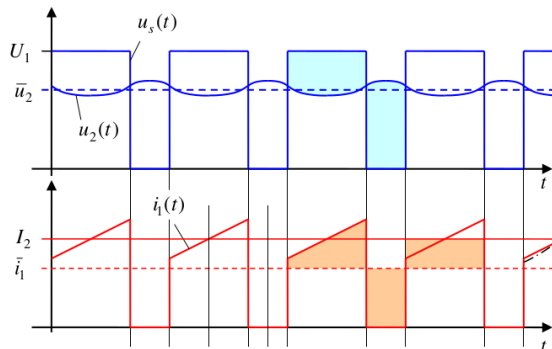Step-down converter with smoothing capacitor²





Power converters convert electrical energy into electrical energy. The conversion (e.g. voltage, current, frequency) is achieved by means of clocked switching.

Other examples:

Switching on/off, AD/DA converter, bicycle light with capacitor, ...



²Schematic diagram and time sequence: Joachim Böcker, GET2, University of Paderborn, modified (abridged)

Comparison of ideal and real switches

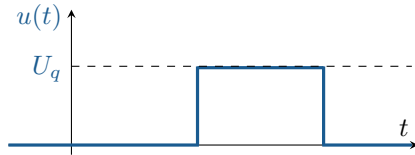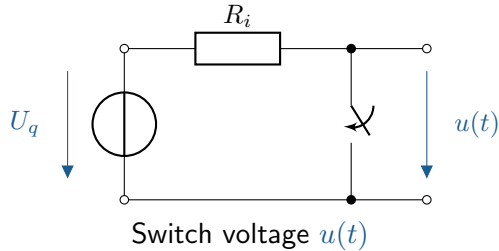


Ideal: lossless, instantaneous

Comparison of ideal and real switches

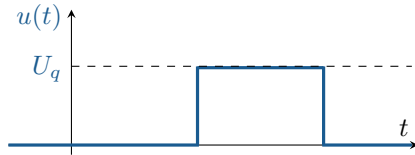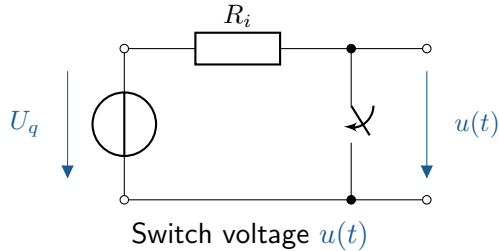


Ideal: lossless, instantaneous

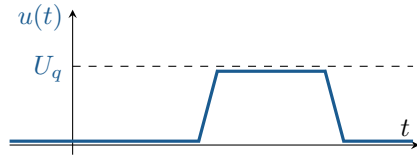

Real: Losses, latencies


Comparison of ideal and real switches

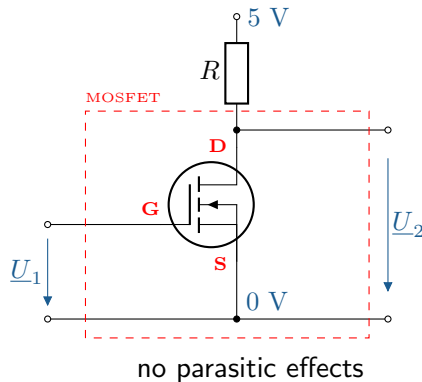


Ideal:

- Here:** Settlement procedures after Switching (switching operations) in focus
- Real:** Settlement procedures during switching
- Confine.:** Assumption of ideal switches

Comparison of ideal and real switches

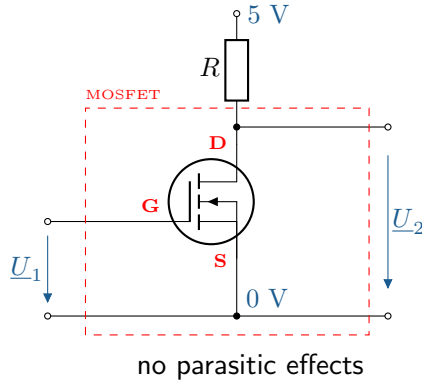

Ideal:

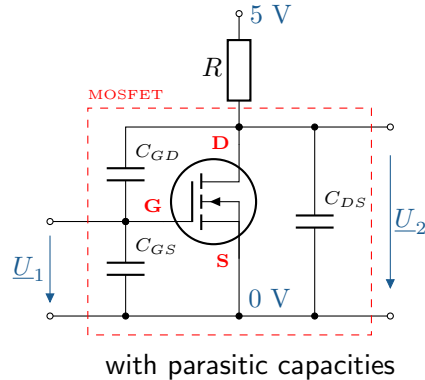

Real:

- | | | |
|------------------|-------------------------------------|---|
| Here: | Settlement procedures <u>after</u> | Switching (switching operations) in focus |
| Real: | Settlement procedures <u>during</u> | switching |
| Confine.: | Assumption of ideal switches | |

Learning objectives: Fundamentals

The students learn:

- ▶ Know and understand fundamental concepts (definitions)
- ▶ Be familiar with calculation methods in the time domain and frequency domain (Laplace)
- ▶ Set up differential equations for circuit quantities of LTI circuits
- ▶ Derive properties of differential equations from circuit properties
- ▶ Determine time responses during switching processes (solve differential equations)

G.	Terms	Definitions
General.	Switch	„set to an (operating) state by pressing a switch“ ^[‡]
	Switch	Component, in this case for opening or closing an electrical connection
Properties	Periodic ¹	„at regular intervals, regularly [occurring, recurring]“ ^[‡]
	Time-invariant ¹	invariant/unchanging over time
	Usually ²	Derivative(s) according to an independent variable (e.g. time t), cf. partial
	Homogeneous ²	Usually in the form: $\sum a_i(t) \frac{d^i}{dt^i} f_i(y(t)) \stackrel{!}{=} 0$ with interference function $b = 0$
	Linear ²	Usually in the form: $\sum a_i(t) \frac{d^i}{dt^i} y(t) = b(t)$ d.h. mit $\frac{d^i}{dt^i} y(t)$ linear
Procedures	Order ²	n [1] i.e. at most derivation of order n in DGL
	Compensation process	Process in a system that strives for a steady state
	Settling-in period	Compensation process, oscillating, endergon (not spontaneous)
	Switching process	non-steady state after switching
	Transient	Compensation process (synonym), cf. transient (adj.)


¹generally

²relating to DGL


[‡]Duden online

Calculation methods for switching operations

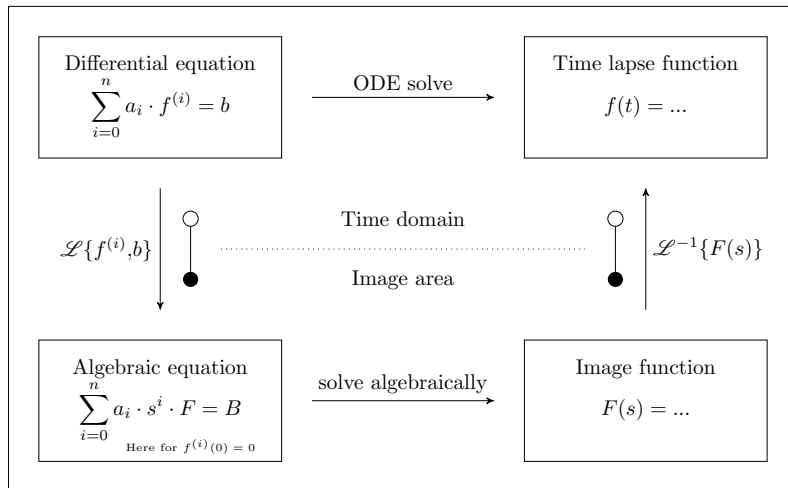
Switching operations can be calculated in the time and image domain.



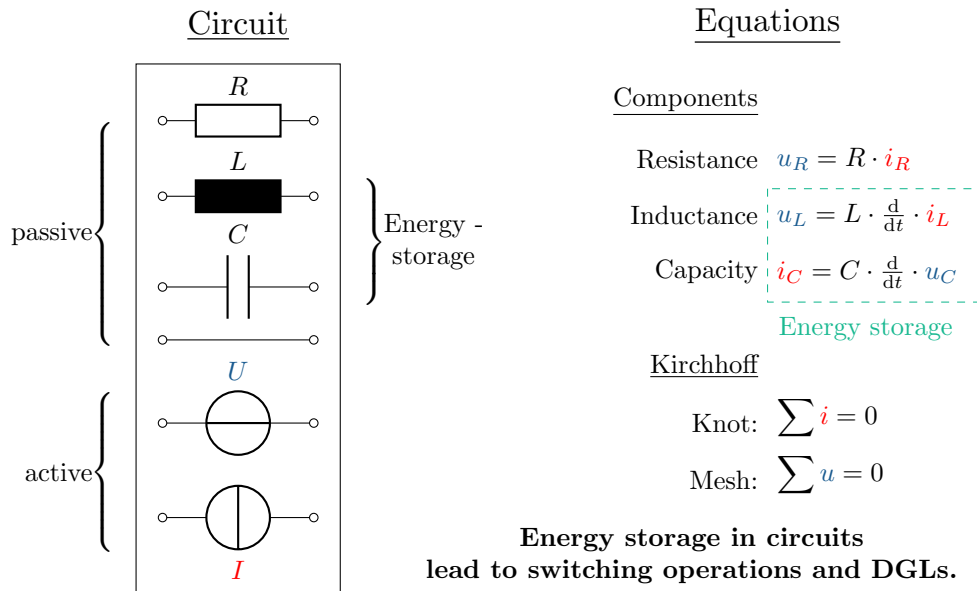
Both methods are based on solving differential equations.



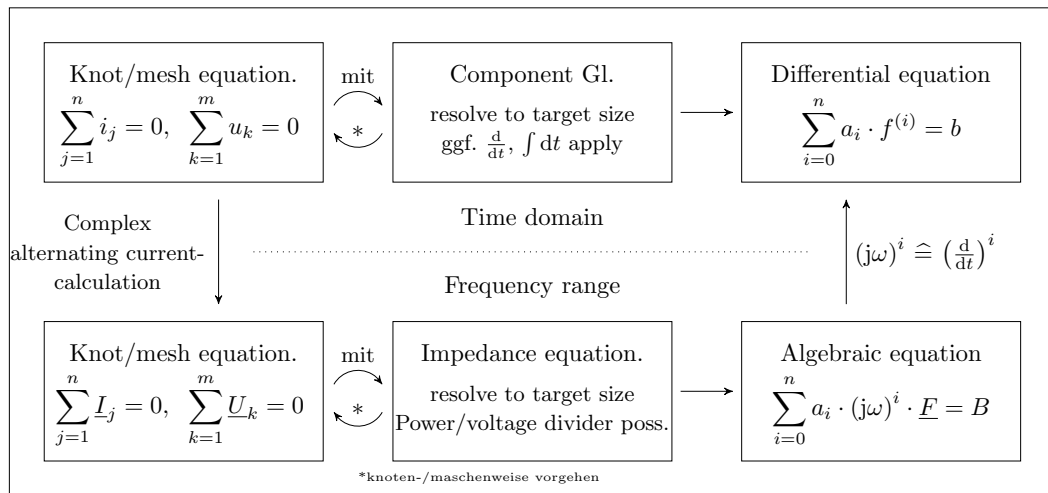Possible approaches to setting up differential equations:



Differential equations set up, example

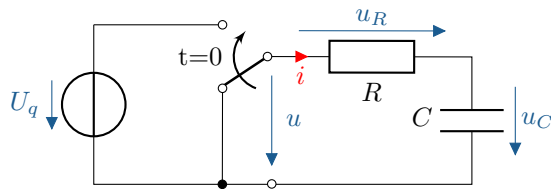

Time domain: Gesucht sei $u_C(t \geq 0)$.

$t \geq 0$

Kirchhoff:

Components:

Knot:

$$i_R = i_C = i$$


$$i_C = C \cdot \frac{d}{dt} u_C$$

Mesh:

$$u_R + u_C = u$$

$$u_R = R \cdot i_R$$

Differential equations set up, example

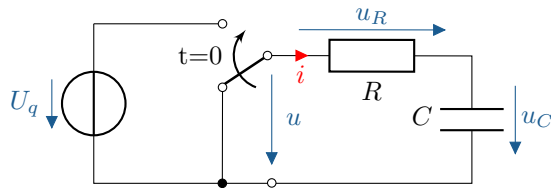

Time domain: Gesucht sei $u_C(t \geq 0)$.

$t \geq 0$

Kirchhoff:

Components:

Knot:

$$i_R = i_C = i$$

$$i_C = C \cdot \frac{d}{dt} u_C$$

Mesh:

$$u_R + u_C = u$$

$$u_R = R \cdot i_R$$

$$R \cdot i + u_C = U_q$$

ODE: $RC \cdot \frac{d}{dt} u_C + u_C = U_q$

1. Ord.

Differential equations set up, example

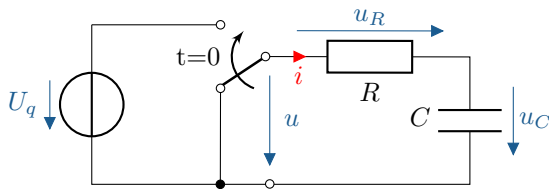



Image area: Wanted $u_C(t \geq 0)$.

$$\underline{U}_C = \underline{U}_q \cdot \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$


$$\left(R + \frac{1}{j\omega C}\right) \cdot \underline{U}_C = \underline{U}_q \cdot \frac{1}{j\omega C}$$

$$(j\omega \cdot RC + 1) \cdot \underline{U}_C = \underline{U}_q$$

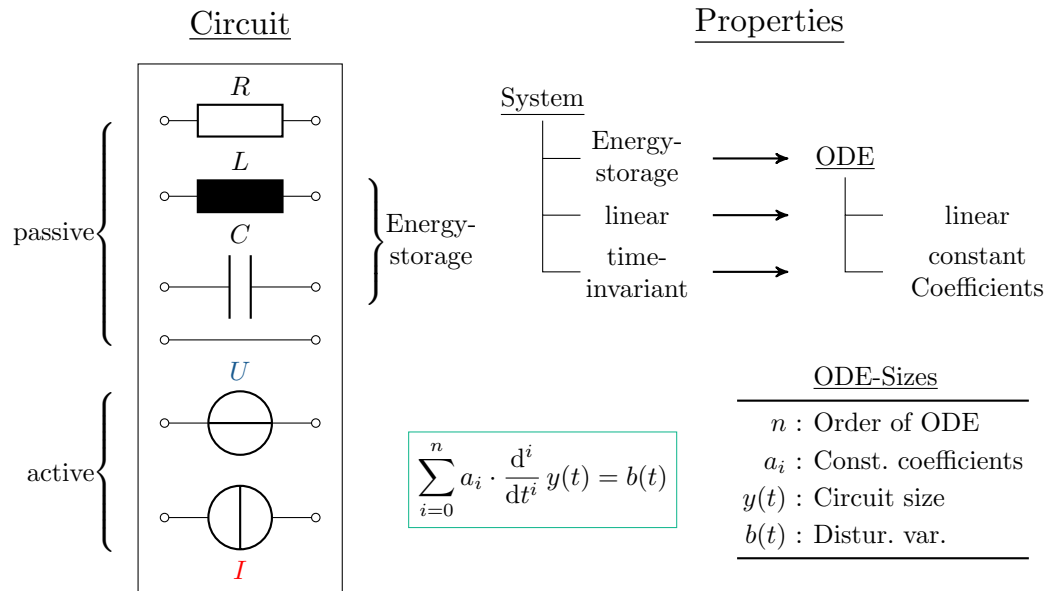
$$\text{DGL : } RC \cdot \frac{d}{dt} u_C + u_C = U_q$$




Order of differential equations

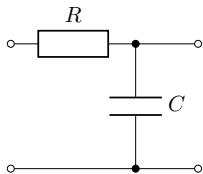


1 En.sp. $\rightarrow$ 1. Ord.

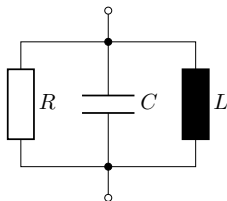

2 En.sp. $\rightarrow$ 2. Ord.

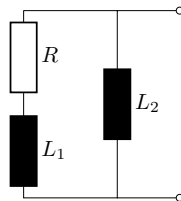

2 En.sp. $\rightarrow$ 2. Ord.

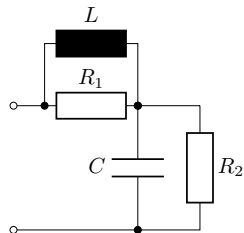

2 En.sp. $\rightarrow$ 2. Ord.

Number of energy storage units[§] = ODE regulations

[§]nicht zusammenfassbar

Every ODE has an infinite number of solutions.

Every ODE has an infinite number of solutions.

A unique solution for ODE n -th order requires n **Initial conditions**.

Every ODE has an infinite number of solutions.

A unique solution for ODE n -th order requires n **Initial conditions**.

Def. Initial conditions: Value of any circuit variable $y(t)$ during switching operation.

Every ODE has an infinite number of solutions.

A unique solution for ODE n -th order requires n **Initial conditions**.

Def. Initial conditions: Value of any circuit variable $y(t)$ during switching operation.

With:

Capacity: $E_{el} = \frac{1}{2}C \cdot u^2 \implies u = \textit{steadily}$ (Electric ener. storage)

Inductance: $E_{mag} = \frac{1}{2}L \cdot i^2 \implies i = \textit{steadily}$ (Mag. ener. storage)

Calculation method in the time domain

Every ODE has an infinite number of solutions.

A unique solution for ODE n -th order requires n **Initial conditions**.

Def. Initial conditions: Value of any circuit variable $y(t)$ during switching operation.

With:

Capacity: $E_{el} = \frac{1}{2}C \cdot u^2 \implies u = \text{steadily}$ (Electric ener. storage)

Inductance: $E_{mag} = \frac{1}{2}L \cdot i^2 \implies i = \text{steadily}$ (Mag. ener. storage)

applies immediately before and after a switching point:


$$\begin{array}{ll} u_{C,t-} = u_{C,t+} & i_{L,t-} = i_{L,t+} \\ \text{with } \lim_{\pm\infty \rightarrow t} u_C(t) = u_{C,t\pm} & \lim_{\pm\infty \rightarrow t} i_L(t) = i_{L,t\pm} \end{array}$$

Decomposition of compensation processes and solution of inhomogeneous differential equations

Disassembly of the **System size** $y(t)$ to:
 steady state $y_e(t)$
and **volatile state** $y_f(t)$.

Decomposition of compensation processes and solution of inhomogeneous differential equations

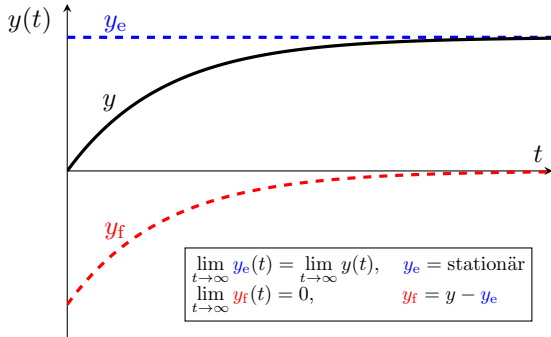Disassembly of the **System size** $y(t)$ to:
steady state $y_e(t)$
and **volatile state** $y_f(t)$.



Decomposition of compensation processes and solution of inhomogeneous differential equations

Disassembly of the **System size** $y(t)$ to:


steady state $y_e(t)$

and **volatile state** $y_f(t)$. and the **general homogeneous solution** y_h

Corresponds to the breakdown of y in:

a **particular solution** y_p

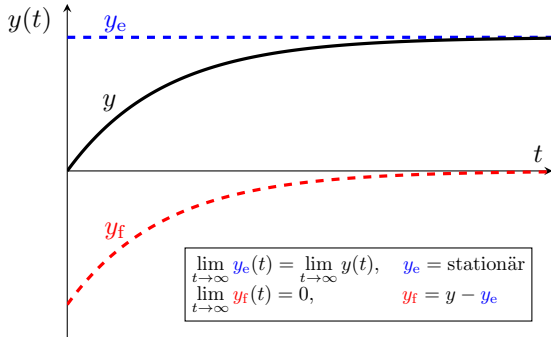and a **general homogeneous solution** y_h



$$y(t) - \underbrace{y_e(t)}_{y_p(t)} = \underbrace{y_f(t)}_{y_h(t)}$$

Decomposition of compensation processes and solution of inhomogeneous differential equations

Disassembly of the **System size** $y(t)$ to:


steady state $y_e(t)$

and **volatile state** $y_f(t)$. and the **general homogeneous solution** y_h

Corresponds to the breakdown of y in:

a **particular solution** y_p

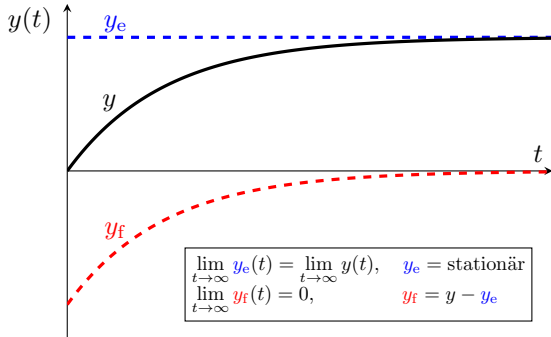and a **general homogeneous solution** y_h



$$y(t) - \underbrace{y_e(t)}_{y_p(t)} = \underbrace{y_f(t)}_{y_h(t)}$$

with

$$\begin{aligned} \sum a_i \cdot \frac{d^i}{dt^i} y &= b(t) \\ - \sum a_i \cdot \frac{d^i}{dt^i} y_e &= b(t) \\ \hline \sum a_i \cdot \frac{d^i}{dt^i} y_f &= 0 \end{aligned}$$

Homogeneous ODE:
$$\sum_{i=0}^n a_i \cdot \frac{d^i}{dt^i} y_h = 0$$

(weighted, linear, const. coeff.)

Calculation of the homogeneous solution

Homogeneous ODE: $\sum_{i=0}^n a_i \cdot \frac{d^i}{dt^i} y_h = 0$ (weighted, linear, const. coeff.)

Approach: $y_h(t) = K \cdot e^{\lambda t}$ (Exponential funct.)

Char. Polynom: $\sum_{i=0}^n a_i \cdot \lambda^i = 0 \Rightarrow \lambda_i = \dots$ (Eigenvalues: λ)

Calculation of the homogeneous solution

Homogeneous ODE: $\sum_{i=0}^n a_i \cdot \frac{d^i}{dt^i} y_h = 0$ (weighted, linear, const. coeff.)

Approach: $y_h(t) = K \cdot e^{\lambda t}$ (Exponential funct.)

Char. Polynom: $\sum_{i=0}^n a_i \cdot \lambda^i = 0 \Rightarrow \lambda_i = \dots$ (Eigenvalues: λ)

1. Solution approach: $y_h(t) = \sum_{i=1}^n K_i \cdot e^{\lambda_i t}$ for $\lambda_i \neq \lambda_{i-1} \forall i$

2. Solution approach: $y_h(t) = \sum_{j=1}^m K_j \cdot t^{j-1} \cdot e^{\lambda t}$ for $\lambda_j = \lambda \forall j$

Calculation of the homogeneous solution

Homogeneous ODE: $\sum_{i=0}^n a_i \cdot \frac{d^i}{dt^i} y_h = 0$ (weighted, linear, const. coeff.)

Approach: $y_h(t) = K \cdot e^{\lambda t}$ (Exponential funct.)

Char. Polynom: $\sum_{i=0}^n a_i \cdot \lambda^i = 0 \Rightarrow \lambda_i = \dots$ (Eigenvalues: λ)

1. Solution approach: $y_h(t) = \sum_{i=1}^n K_i \cdot e^{\lambda_i t}$ for $\lambda_i \neq \lambda_{i-1} \forall i$

2. Solution approach: $y_h(t) = \sum_{j=1}^m K_j \cdot t^{j-1} \cdot e^{\lambda t}$ for $\lambda_j = \lambda \forall j$

gen. homog. solution: $y_h(t) = \dots = y_f$ (Linear combination)

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

The characteristic polynomial:

$$\lambda^5 + 7 \cdot \lambda^4 + 26 \cdot \lambda^3 + 62 \cdot \lambda^2 + 85 \cdot \lambda + 75 = 0$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

The characteristic polynomial:

$$\lambda^5 + 7 \cdot \lambda^4 + 26 \cdot \lambda^3 + 62 \cdot \lambda^2 + 85 \cdot \lambda + 75 = 0$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

The characteristic polynomial:

$$\lambda^5 + 7 \cdot \lambda^4 + 26 \cdot \lambda^3 + 62 \cdot \lambda^2 + 85 \cdot \lambda + 75 = 0$$

has one simple and two double, conjugate, complex zeros:

$$\lambda_1 = -3, \quad \lambda_2 = \lambda_3 = -1 + 2j, \quad \lambda_4 = \lambda_5 = -1 - 2j$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

The characteristic polynomial:

$$\lambda^5 + 7 \cdot \lambda^4 + 26 \cdot \lambda^3 + 62 \cdot \lambda^2 + 85 \cdot \lambda + 75 = 0$$

has one simple and two double, conjugate, complex zeros:

$$\lambda_1 = -3, \quad \lambda_2 = \lambda_3 = -1 + 2j, \quad \lambda_4 = \lambda_5 = -1 - 2j$$

The general solution is:

$$y_h(t) = K_1 \cdot e^{-3t} + (K_2 + K_3 \cdot t) \cdot e^{-t} \sin(2t) + (K_4 + K_5 \cdot t) \cdot e^{-t} \cos(2t)$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

Example: Linearly independent solutions of a differential equation

Find the general solution of the following homogeneous fifth-order differential equation:⁵

$$\frac{d^5}{dt^5}y(t) + 7\frac{d^4}{dt^4}y(t) + 26\frac{d^3}{dt^3}y(t) + 62\frac{d^2}{dt^2}y(t) + 8\frac{d}{dt}y(t) + 75y(t) = 0$$

The characteristic polynomial:

$$\lambda^5 + 7 \cdot \lambda^4 + 26 \cdot \lambda^3 + 62 \cdot \lambda^2 + 85 \cdot \lambda + 75 = 0$$

has one simple and two double, conjugate, complex zeros:

$$\lambda_1 = -3, \quad \lambda_2 = \lambda_3 = -1 + 2j, \quad \lambda_4 = \lambda_5 = -1 - 2j$$

The general solution is:

$$y_h(t) = K_1 \cdot e^{-3t} + (K_2 + K_3 \cdot t) \cdot e^{-t} \sin(2t) + (K_4 + K_5 \cdot t) \cdot e^{-t} \cos(2t)$$

⁵Slightly modified from: Manfred Albach, *Elektrotechnik 2*, Pearson Deutschland GmbH 3. Auflage, 2020.

The **steady state** y_e corresponds to the **particular solution** y_p .

In LZI systems, the following applies:

DC Excitation: $y_p(t) = \text{const.}$ (Equal size)

AC-Excitation: $y_p(t) = \hat{Y} \cdot \sin(\omega t + \varphi)$ (Variable quantity)

This means that the well-known **Network calculation methods** applicable.

DC: Capacities such as open circuits and inductances such as short circuits

AC: Complex alternating current calculation (impedances, admittances)

Key point: Procedure for ODE

1. Set up differential equation (lin., ord.)

$$\sum a_i \cdot \frac{d^i y}{dt^i} = b$$

2. Transient state (homog. sol.)

$$y_f \stackrel{*}{=} \sum K'_i \cdot e^{\lambda_i t}$$

3. Steady-state condition (part. sol.)

$$y_e = y(t \rightarrow \infty)$$

4. Superposition (general sol.)

$$y = y_f + y_e$$

5. Determine constant(s) (initial cond.)

$$i_L, u_C = \text{continuous}$$

*with
$$K'_i = \begin{cases} K_i & \text{for } \lambda_i \neq \lambda_j \quad \forall i, j \\ K_i \cdot t^k & \text{for } \lambda_i = \lambda_{i-k} \quad \text{with } k \in [0, 1, \dots, m-1] \end{cases}$$

(simple NS)

(m -fold zero, k -th identical eigenvalue)

Learning objectives: Switching operations

The students learn:

- ▶ Calculate switching processes in the time domain
- ▶ Know and understand the switching behaviour of RC, RL and RLC elements
- ▶ Know the possibility of minimising switching processes with AC excitation
- ▶ Understand and analyse the oscillation behaviour of oscillating circuits

Switching operations With direct voltage

Switching operations for direct voltage are:

- ▶ Charging operations,
- ▶ Unloading operations.

Switching operations for direct voltage are:

- ▶ Charging operations,
- ▶ Unloading operations.

Calculation initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .

Switching operations for direct voltage are:

- ▶ Charging operations,
- ▶ Unloading operations.

Calculation initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .

RC or RL element $\implies$ **ODE** 1st order

$$a_1 \cdot \frac{d}{dt} y(t) + a_0 \cdot y(t) = b$$

Switching operations With direct voltage

Switching operations for direct voltage are:

- ▶ Charging operations,
- ▶ Unloading operations.


Calculation initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .


RC or RL element $\Rightarrow$ **ODE** 1st order
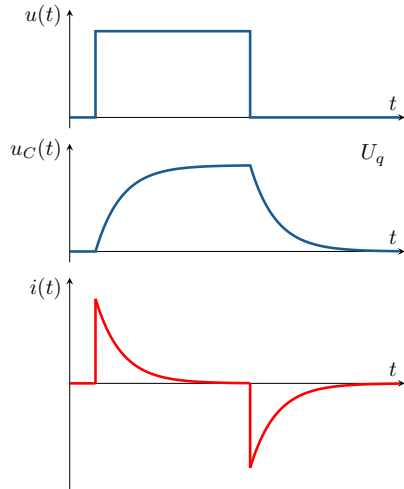
$$a_1 \cdot \frac{d}{dt} y(t) + a_0 \cdot y(t) = b$$




Switching operations in RC circuit (DC)

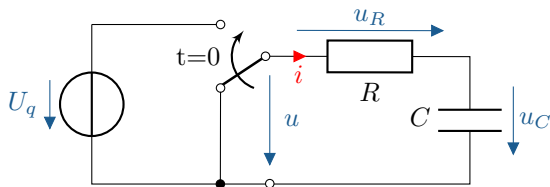Switching operations In terms of capacity, Time constant




First-order ODE $\Rightarrow$ Exponential curve.

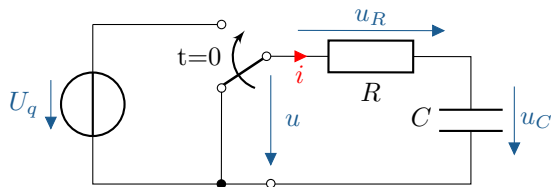Switching operations In terms of capacity, Time constant




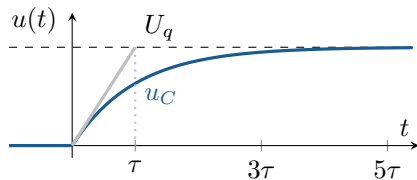First-order ODE $\Rightarrow$ Exponential curve.




$$u_C(t) = U_q (1 - e^{-t/\tau})$$

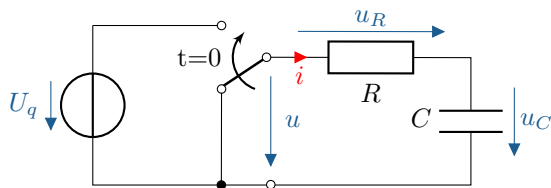Switching operations In terms of capacity, Time constant



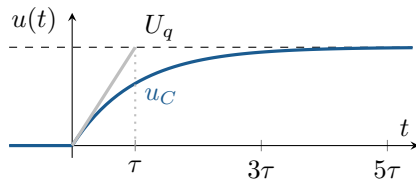First-order ODE $\Rightarrow$ Exponential curve.




$$u_C(t) = U_q (1 - e^{-t/\tau})$$


Die **Time constant** τ , $[\tau] = 1 \text{ s}$:

- determines the steepness of exponential curves.
- is the time after which the tangent reaches its final value.
- is $\tau = RC$ for the RC element.

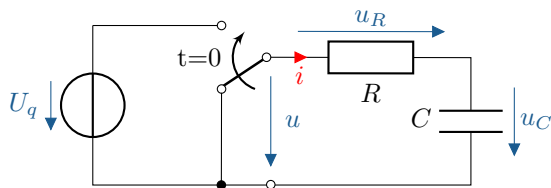Switching operations In terms of capacity, Time constant



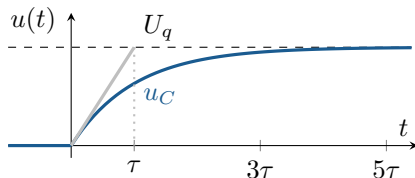First-order ODE $\Rightarrow$ Exponential curve.



$$u_C(t) = U_q (1 - e^{-t/\tau})$$


Die **Time constant** τ , $[\tau] = 1 \text{ s}$:

- determines the steepness of exponential curves.
- is the time after which the tangent reaches its final value.
- is $\tau = RC$ for the RC element.

Typ. values Time constant τ			
t	τ	3τ	5τ
$1 - e^{-t/\tau}$	63,2%	95,0%	99,3%
$e^{-t/\tau}$	36,8%	5,0%	0,7%


Rule of thumb: „Settled in“ to 5τ

Charging process In terms of capacity

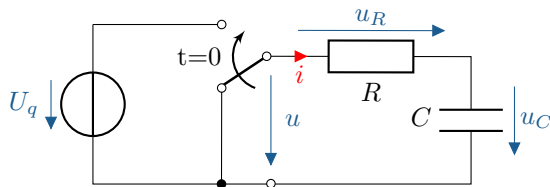

given: $u_C(0)$, U_q , R , C

wanted: $u_C(t)$

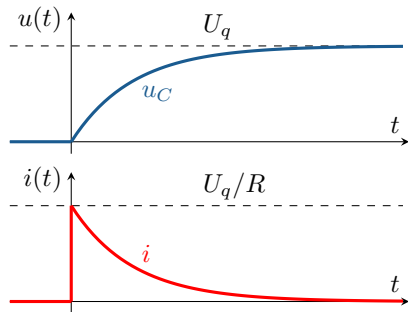

1. ODE

$$U_q = RC \cdot \frac{d}{dt}u_C + u_C$$

2. Homogeneous solution

$$u_{C,h} = K \cdot e^{-t/\tau} \quad \text{with } \tau = RC$$

3. Particular solution

$$u_{C,p} = U_q$$


4. Non-homog. solution

$$u_C = K \cdot e^{-t/\tau} + U_q$$

5. Determine constants

$$u_C = U_q \left(1 - e^{-t/\tau}\right)$$

Charging process In terms of capacity

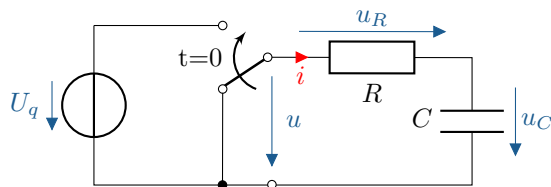


First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for $u_C(t)$ ($t \geq 0$)

Based on the mesh equation, u_R is expressed as a function of u_C :

Charging process In terms of capacity

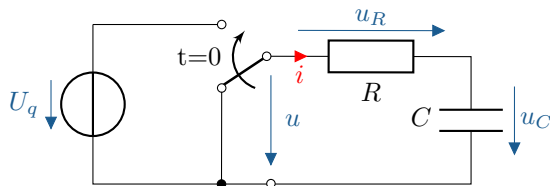

First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for $u_C(t)$ ($t \geq 0$)


Based on the mesh equation, u_R is expressed as a function of u_C :

Kirchhoff :

Mesh: $u_R + u_C = U_q$

Knot: $i_R = i_C = i$

Charging process In terms of capacity

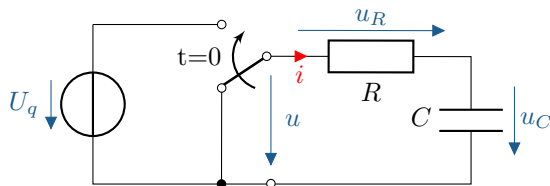

First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for $u_C(t)$ ($t \geq 0$)

Based on the mesh equation, u_R is expressed as a function of u_C :

Kirchhoff :


Mesh: $u_R + u_C = U_q$

Knot: $i_R = i_C = i$

$$R \cdot i + u_C = U_q$$

with $u_R = R \cdot i$

Charging process In terms of capacity

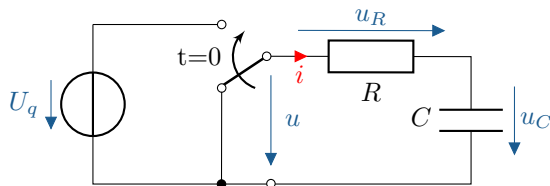

First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for $u_C(t)$ ($t \geq 0$)

Based on the mesh equation, u_R is expressed as a function of u_C :

Kirchhoff : Mesh: $u_R + u_C = U_q$

Knot: $i_R = i_C = i$

$$R \cdot i + u_C = U_q$$

with $u_R = R \cdot i$

ODE : $R \cdot C \cdot \frac{d}{dt}u_C + u_C = U_q$

with $i = C \cdot \frac{d}{dt}u_C$

2.) Homogeneous solution, gen.: (fleeting) (without interference)

$$\text{ODE}_h : \quad RC \cdot \frac{d}{dt} u_{C,h} + u_{C,h} = 0 \quad \text{Approach: } u_{C,h} = K \cdot e^{\lambda t}$$

$$K \cdot (RC \cdot \lambda e^{\lambda t} + e^{\lambda t}) = 0$$

$$\text{char. Polynom:} \quad \Rightarrow \quad RC \cdot \lambda + 1 = 0 \quad \Rightarrow \quad \lambda = -\frac{1}{RC}$$

$$\text{hom. Sol. :} \quad u_{C,h} = K \cdot e^{-t/\tau} \quad \text{with } \tau = RC$$

2.) Homogeneous solution, gen.: (fleeting) (without interference)

$$\text{ODE}_h : \quad RC \cdot \frac{d}{dt} u_{C,h} + u_{C,h} = 0 \quad \text{Approach: } u_{C,h} = K \cdot e^{\lambda t}$$

$$K \cdot (RC \cdot \lambda e^{\lambda t} + e^{\lambda t}) = 0$$

$$\text{char. Polynom:} \quad \Rightarrow \quad RC \cdot \lambda + 1 = 0 \quad \Rightarrow \quad \lambda = -\frac{1}{RC}$$

$$\text{hom. Sol. :} \quad u_{C,h} = K \cdot e^{-t/\tau} \quad \text{with } \tau = RC$$

3. Particular solution: (settled in) (for $t \rightarrow \infty$)

$$\text{ODE}_p : \quad \cancel{RC} \cdot \frac{d}{dt} u_{C,p} + u_{C,p} = U_q \quad \text{with } \left. \frac{d}{dt} \right|_{t \rightarrow \infty} = 0$$

$$\text{part. Sol. :} \quad u_{C,p} = U_q$$

4.) Non-homogenous solution, gen.: (Superimposition)

$$\begin{aligned} \text{gen. sol.:} \quad u_C(t) &= u_{C,h}(t) + u_{C,p}(t) &= u_{C,f}(t) + u_{C,e}(t) \\ u_C(t) &= K \cdot e^{-t/\tau} + U_q \end{aligned}$$

4.) Non-homogenous solution, gen.: (Superimposition)

$$\begin{aligned} u_C(t) &= u_{C,h}(t) + u_{C,p}(t) &= u_{C,f}(t) + u_{C,e}(t) \\ \text{gen. sol.:} \quad u_C(t) &= K \cdot e^{-t/\tau} + U_q \end{aligned}$$

5. Determine constants: (Set initial condition)


$$\text{Initial cond.} \quad u_C(0) = K + U_q \stackrel{!}{=} 0 \quad \Rightarrow \quad K = -U_q$$

$$u_C(t) = -U_q \cdot e^{-t/\tau} + U_q$$

$$\text{special gen. sol.:} \quad u_C(t) = U_q \left(1 - e^{-t/\tau}\right)$$


$$\text{Current:} \quad i_C(t) = \frac{U_q}{R} \cdot e^{-t/\tau} \quad \text{with} \quad i_C = C \cdot \frac{d}{dt} u_C$$

Discharging process In terms of capacity

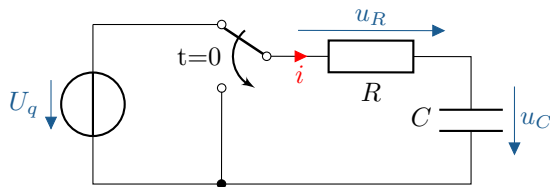

given: $u_C(0), U_q, R, C$

wanted: $u_C(t)$

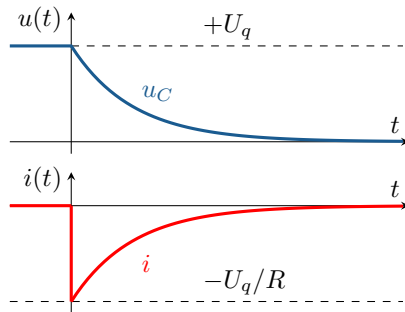

1. ODE

2. Homogeneous solution

3. Particular solution

4. Non-homog. solution

5. Determine constants

$$0 = RC \cdot \frac{d}{dt}u_C + u_C$$


$$u_{C,h} = K \cdot e^{-t/\tau} \quad \text{with } \tau = RC$$

$$u_{C,p} = 0$$

$$u_C = K \cdot e^{-t/\tau}$$

$$u_C = U_q \cdot e^{-t/\tau}$$

Discharging process In terms of capacity

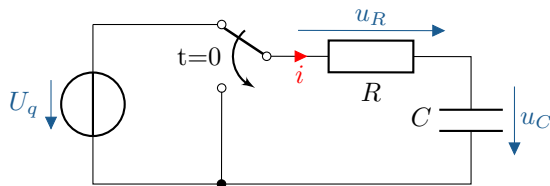

First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for $u_C(t)$ ($t \geq 0$)

Based on the mesh equation, u_R is expressed as a function of u_C :

Kirchhoff : Mesh: $u_R + u_C = 0$

$$R \cdot i + u_C = 0$$

ODE : $RC \cdot \frac{d}{dt}u_C + u_C = 0$

Knot: $i_R = i_C = i$

with $u_R = R \cdot i_R = R \cdot i$

with $i = i_C = C \cdot \frac{d}{dt}u_C$

Discharging process In terms of capacity

2.) Homog. solution, gen.: (fleeting)

$$\text{ODE}_h : \quad RC \cdot \frac{d}{dt} u_{C,h} + u_{C,h} = 0$$

$$\text{Approach: } u_{C,h} = K \cdot e^{\lambda t}$$

$$\text{char. Polynom:} \quad \Rightarrow \quad RC \cdot \lambda + 1 = 0 \quad \Rightarrow \quad \lambda = -\frac{1}{RC}$$

$$\text{hom. Sol. :} \quad u_{C,h} = K \cdot e^{-t/\tau} \quad \text{with } \tau = RC$$

3.) Part. Sol., 4.) Superposition: (settled zero)

$$\text{allg. Lsg.:} \quad u_C = u_{C,h} + \cancel{u_{C,p}} \quad \text{with } u_{C,p} = 0$$



5.) Determine constants: (Insert AB)

$$\text{Initial conditions.} \quad u_C(0) = K \cdot e^0 \stackrel{!}{=} U_q \quad \Rightarrow \quad K = U_q$$

$$\text{special gen. sol.:} \quad u_C(t) = U_q \cdot e^{-t/\tau}$$

$$\text{Current:} \quad i_C(t) = -\frac{U_q}{R} \cdot e^{-t/\tau} \quad \text{with } i_C = C \cdot \frac{d}{dt} u_C$$

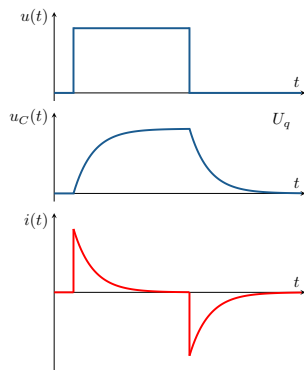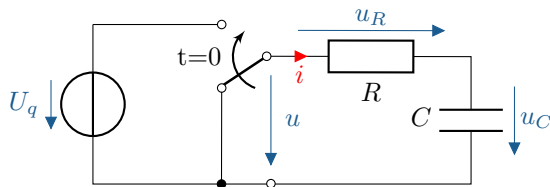Comparison of loading and unloading processes In terms of capacity




Calculation methods are basically the same for (DC) charging and discharging processes.

Voltage u_C after switching time t_0 [see script]:

$$u_C(t - t_0) = \underbrace{u_C(t_0)}_{\text{Initial value}} + \underbrace{(u_{C,e} - u_C(t_0))}_{\text{Difference}} \cdot \underbrace{\left(1 - e^{-\frac{t-t_0}{\tau}}\right)}_{\text{Exp. approximation}}$$


Differences only in the disturbance term of the ODE, initial condition, and final value.

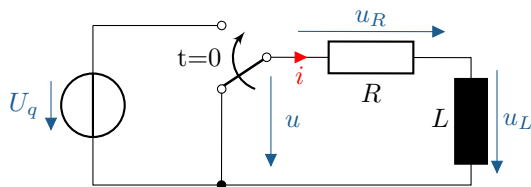Comparison of loading and unloading processes For Inductances



The calculation method for RL elements is basically the same as for RC elements. (First-order ODE) Note: i continuous, u_L discontinuous.

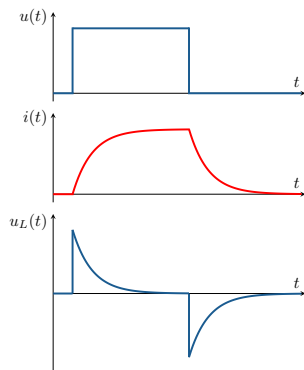
Presumption: Current and voltage „reversed“ relative to RC element.



$$i(t - t_0) = \underbrace{i(t_0)}_{\text{Initial value}} + \underbrace{(i_e - i(t_0))}_{\text{Difference}} \cdot \underbrace{\left(1 - e^{-\frac{t-t_0}{\tau}}\right)}_{\text{Exp. approximation}}$$


Charging: i increasingly, u_L decreasingly. **Discharging:** vice versa.

Charging process For Inductances

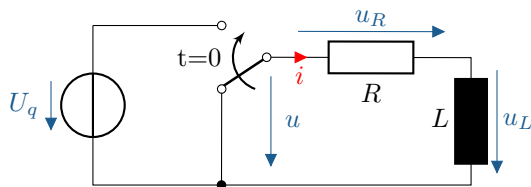

given: $i(0)$, U_q , R , L

wanted: $i(t)$

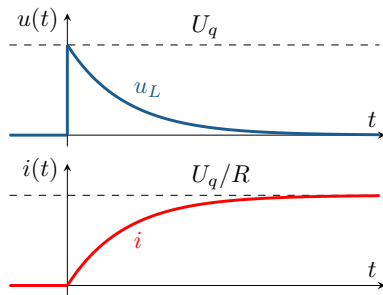

1. ODE

2. Homogeneous Sol.

3. Particular Sol.

4. Non-homogeneous sol.

5. Determine const.

$$\frac{U_q}{R} = \frac{L}{R} \cdot \frac{d}{dt} i + i$$


$$i_h = K \cdot e^{-t/\tau} \quad \text{with} \quad \tau = \frac{L}{R}$$

$$i_p = \frac{U_q}{R}$$

$$i = K \cdot e^{-t/\tau} + \frac{U_q}{R}$$

$$i = \frac{U_q}{R} \left(1 - e^{-t/\tau}\right)$$

Charging process For Inductances

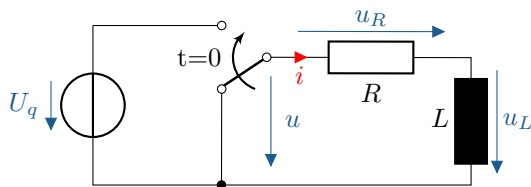

First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1. Set up ODE: for $i(t)$ ($t \geq 0$)

Mesh :

$$u_R + u_L = U_q$$

with $u_R = R \cdot i$

$$R \cdot i + L \cdot \frac{d}{dt}i = U_q$$

with $u_L = L \cdot \frac{d}{dt}i$

$$L \cdot \frac{d}{dt}i + R \cdot i = U_q$$

with $u_L = L \cdot \frac{d}{dt}i$

ODE :

$$\frac{L}{R} \cdot \frac{d}{dt}i + i = \frac{U_q}{R}$$

2.) Homogenous Solution, gen.: (fleeting) (without interference)

$$\text{ODE}_h : \quad \frac{L}{R} \cdot \frac{d}{dt} i_h + i_h = 0$$

$$\text{char. Pol. :} \quad \frac{L}{R} \cdot \lambda + 1 = 0$$

$$\text{hom. Sol. :} \quad i_h = K \cdot e^{-t/\tau}$$

$$\text{Approach: } i_h = K \cdot e^{\lambda t}$$

$$\Rightarrow \lambda = -\frac{1}{\tau} = -\frac{R}{L}$$

$$\text{with } \tau = \frac{L}{R}$$

2.) Homogenous Solution, gen.: (fleeting) (without interference)

$$\text{ODE}_h : \quad \frac{L}{R} \cdot \frac{d}{dt} i_h + i_h = 0$$

$$\text{char. Pol. :} \quad \frac{L}{R} \cdot \lambda + 1 = 0$$

$$\text{hom. Sol. :} \quad i_h = K \cdot e^{-t/\tau}$$

$$\text{Approach: } i_h = K \cdot e^{\lambda t}$$

$$\Rightarrow \lambda = -\frac{1}{\tau} = -\frac{R}{L}$$

$$\text{with } \tau = \frac{L}{R}$$

3.) Particular solution: (settled in) with $t \rightarrow \infty$

$$\text{ODE}_p : \quad \cancel{\frac{L}{R} \cdot \frac{d}{dt}} i_p + i_p = \frac{U_q}{R}$$

$$\text{part. Sol. :} \quad i_p = \frac{U_q}{R}$$

$$\text{with } i_p = \text{const.}$$

4.) Non-homogeneous sol., gen.: (Superimposition)

gener. Sol.:

$$i(t) = \underbrace{K \cdot e^{-t/\tau}}_{i_h} + \underbrace{\frac{U_q}{R}}_{i_p}$$

with $i_h = i_f$, $i_p = i_e$

4.) Non-homogeneous sol., gen.: (Superimposition)

gener. Sol.:
$$i(t) = \underbrace{K \cdot e^{-t/\tau}}_{i_h} + \underbrace{\frac{U_q}{R}}_{i_p} \quad \text{with} \quad i_h = i_f, \quad i_p = i_e$$

5.) Determine constants: (Set initial conditions)


initial cond.
$$i(0) = K \cdot \cancel{e^0} + \frac{U_q}{R} \stackrel{!}{=} 0 \quad \Rightarrow \quad K = -\frac{U_q}{R}$$

clear solution:
$$i(t) = \frac{U_q}{R} \cdot \left(1 - e^{-t/\tau}\right)$$

Determine voltage u_L from current i :


Voltage:
$$u_L = U_q \cdot e^{-t/\tau} \quad \text{with} \quad u_L = L \cdot \frac{d}{dt} i$$

Discharging process For Inductances

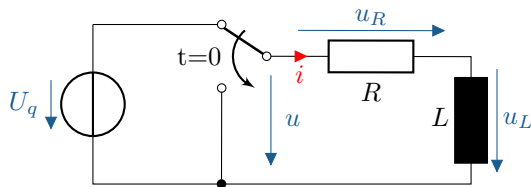

given: $i(0)$, U_q , R , L

wanted: $i(t)$

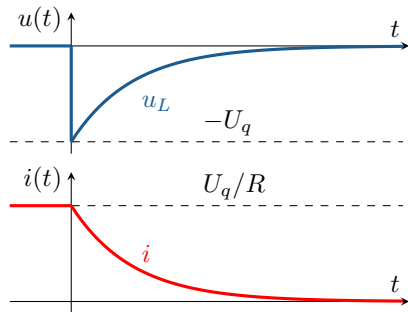

1. ODE

2. Homogenous sol.

3. Particular sol.

4. Non-homogeneous sol.

5. Determine constants

$$0 = \frac{L}{R} \cdot \frac{d}{dt} i + i$$

$$i_h = K \cdot e^{-t/\tau} \quad \text{with} \quad \tau = \frac{L}{R}$$

$$i_p = 0$$

$$i = K \cdot e^{-t/\tau}$$

$$i = \frac{U_q}{R} \cdot e^{-t/\tau}$$

Switching operations with AC excitation are:

- ▶ frequency-dependent (f, ω)
- ▶ switching time dependent (t_0)

Switching operations with AC excitation are:

- ▶ frequency-dependent (f, ω)
- ▶ switching time dependent (t_0)

Calculation analogous to DC, initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .

Switching operations with AC excitation are:

- ▶ frequency-dependent (f, ω)
- ▶ switching time dependent (t_0)

Calculation analogous to DC, initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .

RC or RL element $\implies$ **ODE** 1st order

$$a_1 \cdot \frac{d}{dt} y(t) + a_0 \cdot y(t) = b$$

Switching operations With sinusoidal excitation

Switching operations with AC excitation are:

- ▶ frequency-dependent (f, ω)
- ▶ switching time dependent (t_0)


Calculation analogous to DC, initially for:

- ▶ a capacity C
- ▶ an inductance L

each in series with a resistor R .


RC or RL element $\implies$ **ODE** 1st order
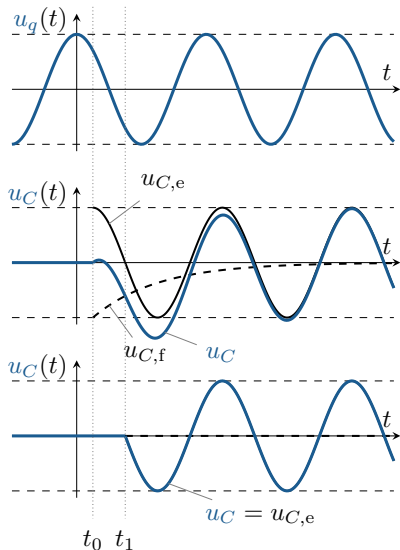
$$a_1 \cdot \frac{d}{dt} y(t) + a_0 \cdot y(t) = b$$



Comparison: switching times t_0 and t_1

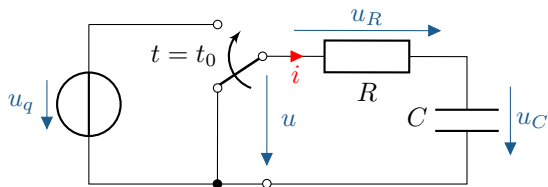
Switching operations With sinusoidal excitation In terms of capacity



given: $u_C(t_0)$, $u_q(t)$, R , C , ω


wanted: $u_C(t)$ for $t \geq t_0$

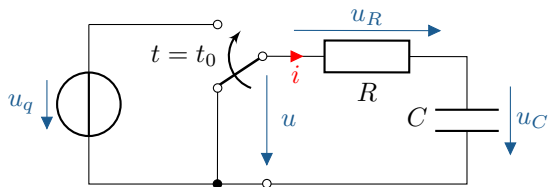Switching operations With sinusoidal excitation In terms of capacity




given: $u_C(t_0)$, $u_q(t)$, R , C , ω

wanted: $u_C(t)$ for $t \geq t_0$

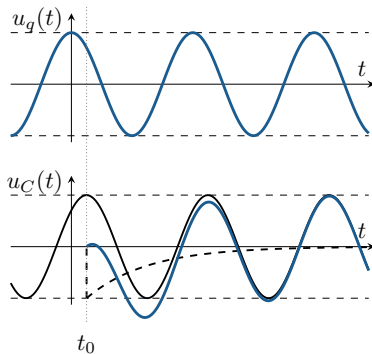


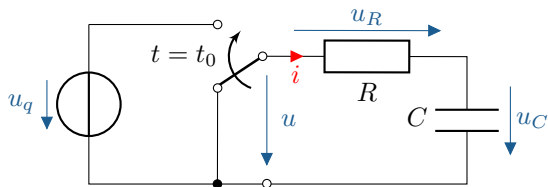Switching operations With sinusoidal excitation In terms of capacity



given: $u_C(t_0)$, $u_q(t)$, R , C , ω

wanted: $u_C(t)$ for $t \geq t_0$

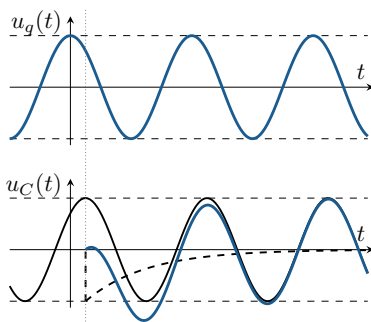

1. ODE

$$u_q = RC \cdot \frac{d}{dt} u_C(t) + u_C(t) = \hat{U}_q \cdot \cos(\omega t + \varphi_q)$$

2. Homogeneous solution

$$u_{C,h} = K \cdot e^{-\frac{t-t_0}{\tau}} \quad \text{with} \quad \tau = RC$$

3. Particular solution

$$u_{C,p} = \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p})$$


4. Inhomogeneous solutiong

$$u_C = K \cdot e^{-\frac{t-t_0}{\tau}} + \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p})$$

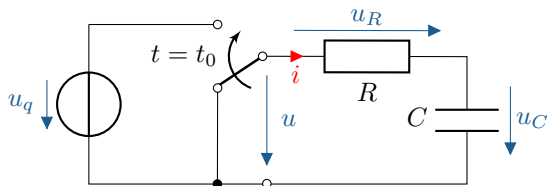5. Determine constants

$$u_C = \hat{U}_{C,p} \cdot \left(-\cos(\omega t_0 + \varphi_{C,p}) \cdot e^{-\frac{t-t_0}{\tau}} + \cos(\omega t + \varphi_{C,p}) \right)$$

Switching operations With sinusoidal excitation In terms of capacity



First-order ODE:


$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for u_c ($t \geq t_0$)

$$RC \cdot \frac{d}{dt}u_C(t) + u_C(t) = u_q(t)$$

$$\text{with } u_q(t) = \hat{U}_q \cdot \cos(\omega t + \varphi_q) \quad (\text{Disturbance})$$

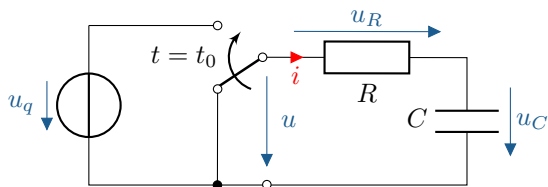Switching operations With sinusoidal excitation In terms of capacity



First-order ODE:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for u_c ($t \geq t_0$)

$$RC \cdot \frac{d}{dt}u_C(t) + u_C(t) = u_q(t)$$

$$\text{with } u_q(t) = \hat{U}_q \cdot \cos(\omega t + \varphi_q) \quad (\text{Disturbance})$$

2.) Homogeneous solution, general (fleeting) (without interference):

$$u_{C,h} = K \cdot e^{-\frac{t'}{\tau}}$$

$$\text{with } t' = t - t_0$$

$$= K \cdot e^{-\frac{t-t_0}{\tau}}$$

$$\text{with } \tau = RC$$

3.) **Particular solution** (settled in) ($t \rightarrow \infty$): sinusoidal!

Application of complex alternating current calculation:

$$\begin{aligned} u_{C,p} &= \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p}) \\ &= \operatorname{Re} \left\{ \underline{\hat{U}}_{C,p} \cdot e^{j\omega t} \right\} \quad \text{with} \quad \underline{\hat{U}}_{C,p} = \hat{U}_{C,p} \cdot e^{j\varphi_{C,p}} \end{aligned}$$

3.) Particular solution (settled in) ($t \rightarrow \infty$): sinusoidal!

Application of complex alternating current calculation:

$$\begin{aligned} u_{C,p} &= \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p}) \\ &= \operatorname{Re} \left\{ \underline{\hat{U}}_{C,p} \cdot e^{j\omega t} \right\} \quad \text{with} \quad \underline{\hat{U}}_{C,p} = \hat{U}_{C,p} \cdot e^{j\varphi_{C,p}} \end{aligned}$$

Complex amplitude indicator $\underline{\hat{U}}_{C,p}$ using complex voltage divider:

$$\underline{\hat{U}}_{C,p} = \underline{\hat{U}}_q \cdot \frac{\underline{Z}_C}{R + \underline{Z}_C} = \underline{\hat{U}}_q \cdot \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{\underline{\hat{U}}_q}{1 + j\omega CR} \quad \text{with} \quad \underline{\hat{U}}_q = \hat{U}_q \cdot e^{j\varphi_q}$$

3.) Particular solution (settled in) ($t \rightarrow \infty$): sinusoidal!

Application of complex alternating current calculation:

$$\begin{aligned} u_{C,p} &= \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p}) \\ &= \operatorname{Re} \left\{ \underline{\hat{U}}_{C,p} \cdot e^{j\omega t} \right\} \quad \text{with} \quad \underline{\hat{U}}_{C,p} = \hat{U}_{C,p} \cdot e^{j\varphi_{C,p}} \end{aligned}$$

Complex amplitude indicator $\underline{\hat{U}}_{C,p}$ using complex voltage divider:

$$\underline{\hat{U}}_{C,p} = \underline{\hat{U}}_q \cdot \frac{\underline{Z}_C}{R + \underline{Z}_C} = \underline{\hat{U}}_q \cdot \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{\underline{\hat{U}}_q}{1 + j\omega CR} \quad \text{with} \quad \underline{\hat{U}}_q = \hat{U}_q \cdot e^{j\varphi_q}$$

For the amplitude $\hat{U}_{C,p}$ and the (load) phase angle $\varphi_{C,p}$, the following applies:

$$\hat{U}_{C,p} = \frac{\hat{U}_q}{\sqrt{1 + (\omega CR)^2}} \quad \text{und} \quad \varphi_{C,p} = \varphi_q - \arctan(\omega CR)$$

4.) Inhomogeneous solution, general (Superposition):

$$\begin{aligned}u_C &= u_{C,h} + u_{C,p} \\ &= K \cdot e^{-\frac{t-t_0}{\tau}} + \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p})\end{aligned}$$

5.) Determine constants (Initial condition):

$$\begin{aligned}u_C(t_0) &\stackrel{!}{=} 0 \\ K \cdot \cancel{e^0} + \hat{U}_{C,p} \cdot \cos(\omega t_0 + \varphi_{C,p}) &= 0 \\ K &= -\hat{U}_{C,p} \cdot \cos(\omega t_0 + \varphi_{C,p})\end{aligned}$$

4.) Inhomogeneous solution, general (Superposition):

$$\begin{aligned}u_C &= u_{C,h} + u_{C,p} \\ &= K \cdot e^{-\frac{t-t_0}{\tau}} + \hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p})\end{aligned}$$

5.) Determine constants (Initial condition):

$$\begin{aligned}u_C(t_0) &\stackrel{!}{=} 0 \\ K \cdot \cancel{e^0} + \hat{U}_{C,p} \cdot \cos(\omega t_0 + \varphi_{C,p}) &= 0 \\ K &= -\hat{U}_{C,p} \cdot \cos(\omega t_0 + \varphi_{C,p})\end{aligned}$$

The unique solution is obtained by substituting K into the general solution:

$$u_C(t) = \underbrace{-\hat{U}_{C,p} \cdot \cos(\omega t_0 + \varphi_{C,p}) \cdot e^{-\frac{t-t_0}{\tau}}}_{u_{C,h}} + \underbrace{\hat{U}_{C,p} \cdot \cos(\omega t + \varphi_{C,p})}_{u_{C,p}}$$

Switching operations With sinusoidal excitation In terms of capacity

For sinusoidal excitation:

With large time constants,
overvoltages/overcurrents are possible.

For sinusoidal excitation:

With large time constants,
overvoltages/overcurrents are possible.

Excess values of up to twice/three times
the peak
value can be reached.

For sinusoidal excitation:

With large time constants,
overvoltages/overcurrents are possible.

Excess values of up to twice/three times
the peak
value can be reached.

By shifting gears skillfully,
Compensation transactions avoidable.

Switching operations With sinusoidal excitation In terms of capacity


For sinusoidal excitation:

With large time constants,
overvoltages/overcurrents are possible.

Excess values of up to twice/three times
the peak
value can be reached.


By shifting gears skillfully,
Compensation transactions avoidable.

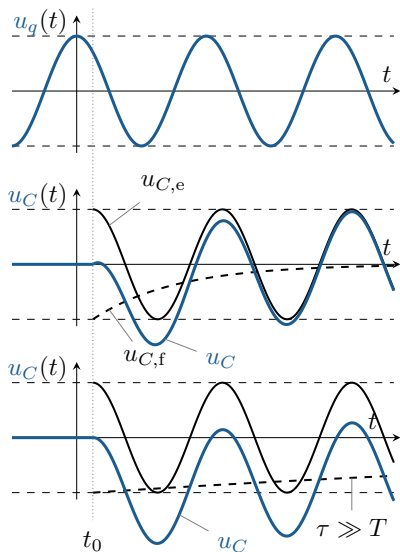Example: Disconnect switch in the network



Comparison: small and large τ

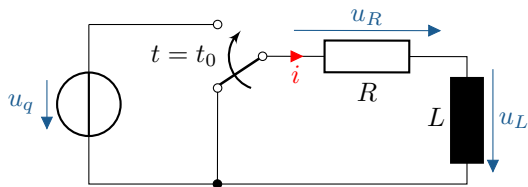
Switching operations With sinusoidal excitation For Inductors



given: $i(t_0)$, $u_q(t)$, R , L , ω


wanted: $i(t)$ for $t \geq t_0$

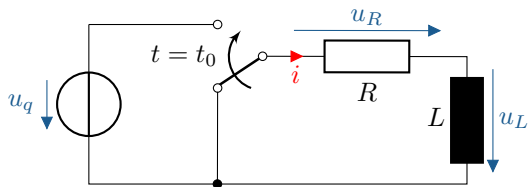Switching operations With sinusoidal excitation For Inductors




given: $i(t_0)$, $u_q(t)$, R , L , ω

wanted: $i(t)$ for $t \geq t_0$

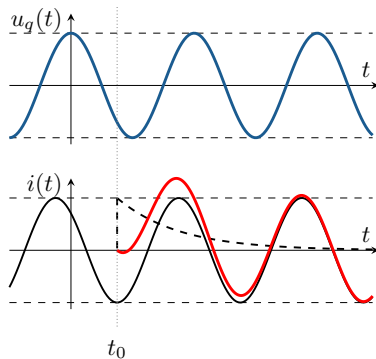


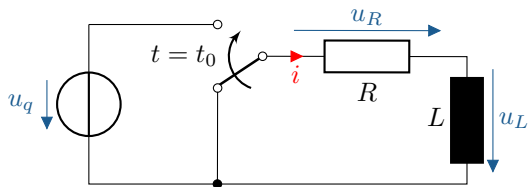Switching operations With sinusoidal excitation For Inductors



given: $i(t_0)$, $u_q(t)$, R , L , ω

wanted: $i(t)$ for $t \geq t_0$

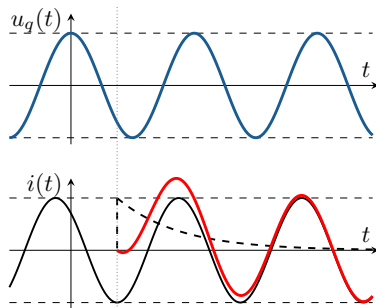

1. ODE

$$\frac{u_q}{R} = \frac{L}{R} \cdot \frac{d}{dt} i + i = \frac{\hat{U}_q}{R} \cdot \cos(\omega t + \varphi_q)$$

2. Homogeneous sol.

$$i_h = K \cdot e^{-\frac{t-t_0}{\tau}} \quad \text{with} \quad \tau = \frac{L}{R}$$

3. Particular sol.

$$i_p = \hat{I}_p \cdot \cos(\omega t + \varphi_I)$$


4. Non-homogeneous sol.

$$i = K \cdot e^{-\frac{t-t_0}{\tau}} + \hat{I}_p \cdot \cos(\omega t + \varphi_I)$$

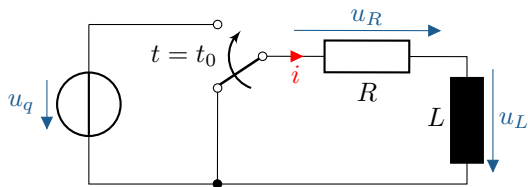5. Determine constants

$$i = \hat{I}_p \cdot \left(-\cos(\omega t_0 + \varphi_I) \cdot e^{-\frac{t-t_0}{\tau}} + \cos(\omega t + \varphi_I) \right)$$

Switching operations With sinusoidal excitation For Inductors



ODE 1st order:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$


1.) Set up ODE: for i with $t \geq t_0$

ODE :

$$\frac{L}{R} \cdot \frac{d}{dt}i + i = \frac{u_q}{R}$$

with $u_q = \hat{U}_q \cdot \cos(\omega t + \varphi_q)$

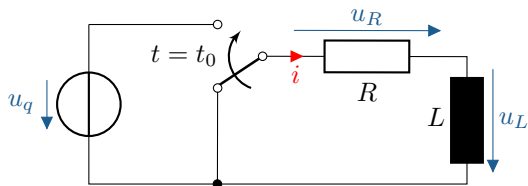Switching operations With sinusoidal excitation For Inductors



ODE 1st order:

$$a_1 \cdot \frac{d}{dt}y(t) + a_0 \cdot y(t) = b$$

1.) Set up ODE: for i with $t \geq t_0$

$$\text{ODE :} \quad \frac{L}{R} \cdot \frac{d}{dt}i + i = \frac{u_q}{R}$$

$$\text{with } u_q = \hat{U}_q \cdot \cos(\omega t + \varphi_q)$$

2.) Homogeneous solution, gen.: (fleeting, for switching time t_0)

$$\text{hom. Sol.:} \quad i_h = K \cdot e^{-\frac{t-t_0}{\tau}} \quad \text{with } \tau = \frac{L}{R}$$

3.) Particular solution: (settled in, with $t \rightarrow \infty$)

ODE transf. : $\frac{L}{R} \cdot j\omega \hat{\underline{i}}_p + \hat{\underline{i}}_p = \frac{\hat{\underline{U}}_q}{R}$ with $\hat{\underline{U}}_q = \hat{U}_q \cdot e^{j\varphi_q}$

Pointer: $\hat{\underline{i}}_p = \frac{\hat{\underline{U}}_q}{R} \cdot \frac{1}{1 + j\omega \cdot \frac{L}{R}}$ with $\hat{\underline{i}}_p = \hat{I}_p \cdot e^{j\varphi_I}$

$$\hat{I}_p = \frac{\hat{U}_q}{R} \cdot \frac{1}{\sqrt{1 + \left(\omega \cdot \frac{L}{R}\right)^2}}$$

$$\varphi_I = \varphi_q - \arctan\left(\omega \cdot \frac{L}{R}\right)$$

part. Sol. : $i_p = \hat{I}_p \cdot \cos(\omega t + \varphi_I)$ with $i_p = \operatorname{Re} \left\{ \hat{\underline{i}}_p \cdot e^{j\omega t} \right\}$

4.) Non-homogeneous solution, gen.: (Superposition)

Gen. Sol.:

$$\dot{i} = \underbrace{K \cdot e^{-\frac{t-t_0}{\tau}}}_{i_h} + \underbrace{\hat{I}_p \cdot \cos(\omega t + \varphi_I)}_{i_p}$$

4.) Non-homogeneous solution, gen.: (Superposition)

Gen. Sol.:

$$i = \underbrace{K \cdot e^{-\frac{t-t_0}{\tau}}}_{i_h} + \underbrace{\hat{I}_p \cdot \cos(\omega t + \varphi_I)}_{i_p}$$

5.) Determine constants: (Insert AB)

Initial requi.:

$$i(t_0) = K \cdot e^0 + \hat{I}_p \cdot \cos(\omega t_0 + \varphi_I) \stackrel{!}{=} 0$$

$$\Rightarrow K = -\hat{I}_p \cdot \cos(\omega t_0 + \varphi_I)$$

single sol.:

$$i(t) = -\hat{I}_p \cdot \cos(\omega t_0 + \varphi_I) \cdot e^{-\frac{t-t_0}{\tau}} + \hat{I}_p \cdot \cos(\omega t + \varphi_I)$$

4.) Non-homogeneous solution, gen.: (Superposition)

Gen. Sol.:
$$i = \underbrace{K \cdot e^{-\frac{t-t_0}{\tau}}}_{i_h} + \underbrace{\hat{I}_p \cdot \cos(\omega t + \varphi_I)}_{i_p}$$

5.) Determine constants: (Insert AB)


Initial requi.:
$$i(t_0) = K \cdot e^0 + \hat{I}_p \cdot \cos(\omega t_0 + \varphi_I) \stackrel{!}{=} 0$$
$$\Rightarrow K = -\hat{I}_p \cdot \cos(\omega t_0 + \varphi_I)$$

single sol.:
$$i(t) = -\hat{I}_p \cdot \cos(\omega t_0 + \varphi_I) \cdot e^{-\frac{t-t_0}{\tau}} + \hat{I}_p \cdot \cos(\omega t + \varphi_I)$$


Voltage u_L with $u_L = L \cdot \frac{d}{dt} i$ calculate:

Voltage:
$$u_L(t) = R \cdot \hat{I}_p \cdot \cos(\omega t_0 + \varphi_I) \cdot e^{-\frac{t-t_0}{\tau}} - \omega L \cdot \hat{I}_p \cdot \sin(\omega t + \varphi_I)$$

RLC series resonant circuits

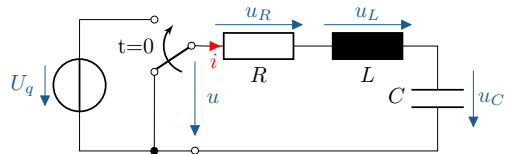

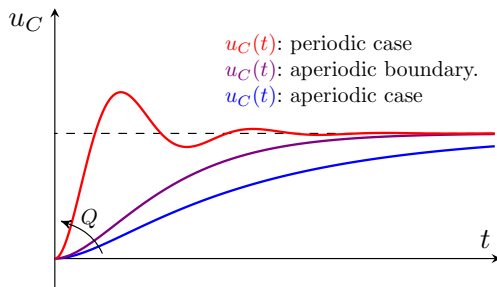Because of L and $C \Rightarrow$ oscillating circuit




ODE (for u_C for $t \geq 0$):

$$LC \cdot \frac{d^2}{dt^2} u_C + RC \cdot \frac{d}{dt} u_C + u_C = U_q$$

Case differentiation	Damping	Discri.	Güte
Aperiodic case	strong	$D > 0$	$Q < 0.5$
Aperiodic borderline case	critical	$D = 0$	$Q = 0.5$
Periodic case	weak	$D < 0$	$Q > 0.5$

RLC series resonant circuits

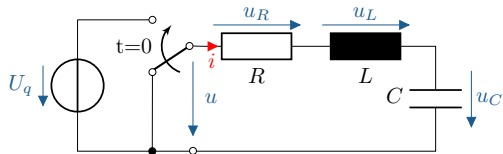

Approach: $u_{C,h} = K \cdot e^{\lambda t}$

1.) ODE: $u_L + u_R + u_C = u$

$$L \cdot \frac{d}{dt} i + R \cdot i + u_C = U_q$$

$$LC \cdot \frac{d^2}{dt^2} u_C + RC \cdot \frac{d}{dt} u_C + u_C = U_q$$

homogeneous ODE:

$$LC \cdot \frac{d^2}{dt^2} u_{C,h} + RC \cdot \frac{d}{dt} u_{C,h} + u_{C,h} = 0$$


char. Polynom:

$$\lambda^2 + \frac{R}{L} \cdot \lambda + \frac{1}{LC} = 0$$

Eigenvalue:

$$\lambda_{1/2} = -\frac{R}{2L} \pm \underbrace{\sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}_{\text{Discriminant } D}$$

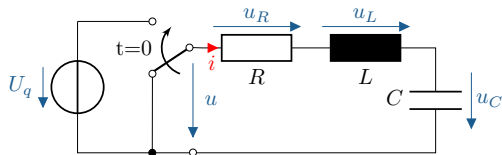
Case differentiation for RLC series resonant circuits



$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Attention! Depending on the discriminant D , different eigenvalues $\lambda_{1/2}$.

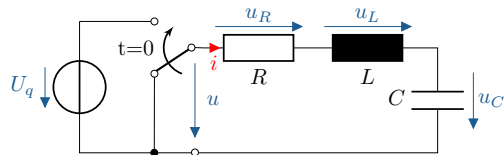Case differentiation for RLC series resonant circuits




$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Attention! Depending on the discriminant D , different eigenvalues $\lambda_{1/2}$.

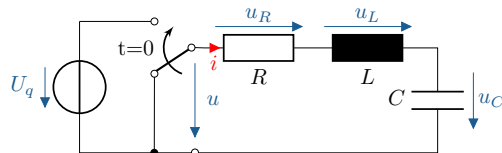2.) Homogeneous solution:

$$u_{C,h} = \begin{cases} K_1 \cdot e^{\lambda_1 t} + K_2 \cdot e^{\lambda_2 t} & \text{for } \lambda_1 \neq \lambda_2 \\ (K_1 + K_2 \cdot t) \cdot e^{\lambda t} & \text{for } \lambda_1 = \lambda_2 = \lambda \end{cases}$$

Case differentiation for RLC series resonant circuits



$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$


Attention! Depending on the discriminant D , different eigenvalues $\lambda_{1/2}$.

2.) Homogeneous solution:

$$u_{C,h} = \begin{cases} K_1 \cdot e^{\lambda_1 t} + K_2 \cdot e^{\lambda_2 t} & \text{for } \lambda_1 \neq \lambda_2 \\ (K_1 + K_2 \cdot t) \cdot e^{\lambda t} & \text{for } \lambda_1 = \lambda_2 = \lambda \end{cases}$$

Case differentiation	Discrimi.	Eigenvalue $\lambda_{1/2}$
aperiodic case	$D > 0$	Two different, real NSTs
aperiodic borderline case	$D = 0$	A double, real NST
periodic case	$D < 0$	Two conjugated, complex NSTs

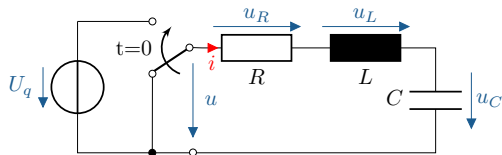Aperiodic case in the RLC series resonant circuit




$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Aperiodic case (Creep case)

with $D > 0$ applies

$$\frac{R}{2L} \stackrel{!}{>} \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \quad \Rightarrow \quad 2 \text{ real eigenvalues}$$

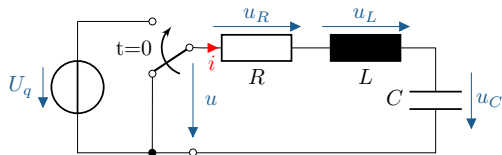Aperiodic case in the RLC series resonant circuit



$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Aperiodic case (Creep case)

with $D > 0$ applies $\frac{R}{2L} > \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} \Rightarrow 2 \text{ real eigenvalues}$

2.) Homogeneous solution: (fleeting)

$$u_{C,h} = K_1 \cdot e^{\lambda_1 t} + K_2 \cdot e^{\lambda_2 t} \quad \text{with } \lambda_1 \neq \lambda_2, \lambda < 0 \quad (1)$$

3.) Particular solution: (settled, identical for all three cases)

$$u_{C,p} = U_q$$

4.) General solution: (Superposition)

$$u_C(t) = K_1 \cdot e^{\lambda_1 t} + K_2 \cdot e^{\lambda_2 t} + U_q$$

4.) General solution: (Superposition)

$$u_C(t) = K_1 \cdot e^{\lambda_1 t} + K_2 \cdot e^{\lambda_2 t} + U_q$$

5.) Determine constants: (as is known)


Initial conditions (AB): $u_C(0) = 0$ and $i(0) = 0 \Rightarrow \frac{d}{dt} u_C(0) = 0$

$$\text{1st IC: } u_C(0) = K_1 \cdot e^{\cancel{\lambda_1 0}} + K_2 \cdot e^{\cancel{\lambda_2 0}} + U_q \stackrel{!}{=} 0 \quad \Rightarrow \quad K_1 = -K_2 - U_q$$

$$\text{2nd IC: } \frac{d}{dt} u_C(0) = K_1 \cdot \lambda_1 \cdot e^{\cancel{\lambda_1 0}} + K_2 \cdot \lambda_2 \cdot e^{\cancel{\lambda_2 0}} + \cancel{0} \stackrel{!}{=} 0 \quad \Rightarrow \quad K_1 = -K_2 \frac{\lambda_2}{\lambda_1}$$

$$\Rightarrow \quad K_1 = \frac{U_q}{\frac{\lambda_1}{\lambda_2} - 1} \quad \text{and} \quad K_2 = \frac{U_q}{\frac{\lambda_2}{\lambda_1} - 1}$$

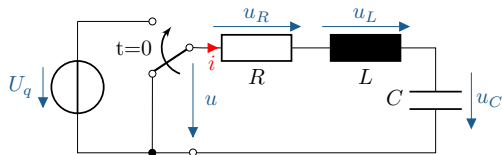Aperiodic boundary case in the RLC series resonant circuit




$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Aperiodic borderline case:

for $D = 0$ applies $\lambda_{1/2} = -\frac{R}{2L} \pm \cancel{\sqrt{0}} = \lambda \quad \Rightarrow \quad 1 \text{ real Eigenvalue}$

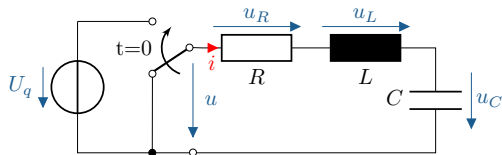Aperiodic boundary case in the RLC series resonant circuit



$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

Aperiodic borderline case:

for $D = 0$ applies $\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{0} = \lambda \Rightarrow 1 \text{ real Eigenvalue}$

2.) Homogeneous solution: (fleeting)

$$u_{C,h} = (K_1 + K_2 \cdot t) \cdot e^{\lambda t} \quad \text{with } \lambda_1 = \lambda_2 < 0 \quad (2)$$

3.) Particular solution: (settled in)

$$u_{C,p} = U_q$$

4.) General solution: (settled in)


$$u_C(t) = (K_1 + K_2 \cdot t) \cdot e^{\lambda t} + U_q$$

5.) Determine constants: (as is known)

Initial conditions (AB): $u_C(0) = 0$ and $i(0) = 0 \Rightarrow \frac{d}{dt} u_C(0) = 0$

$$\begin{aligned} \text{1st IC:} \quad u_C(0) &= (K_1 + \cancel{K_2 \cdot 0}) \cdot \cancel{e^{\lambda 0}} + U_q \stackrel{!}{=} 0 & \Rightarrow \quad K_1 &= -U_q \\ \text{2nd IC:} \quad \frac{d}{dt} u_C(0) &= (K_1 + \cancel{K_2 \cdot 0}) \cdot \lambda \cdot \cancel{e^{\lambda 0}} + K_2 \cdot \cancel{e^{\lambda 0}} \stackrel{!}{=} 0 & \Rightarrow \quad K_2 &= -K_1 \cdot \lambda \\ \Rightarrow \quad & K_1 = -U_q \quad \text{and} \quad K_2 = +U_q \cdot \lambda \end{aligned}$$

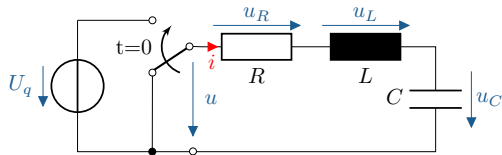Periodic case for the RLC series resonant circuit




$$\lambda_{1/2} = -\frac{R}{2L} \pm \underbrace{\sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}_{\text{Discriminant } D}$$

Periodic case: (swing fall)

for $D < 0$ applies $\lambda_{1/2} = \underbrace{-\frac{R}{2L}}_{\delta} \pm j \cdot \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}_{\omega_d} \Rightarrow 2 \text{ compl. EW}$

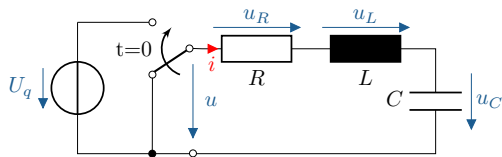(3)

Periodic case for the RLC series resonant circuit



$$\lambda_{1/2} = -\frac{R}{2L} \pm \underbrace{\sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}_{\text{Discriminant } D}$$

Periodic case: (swing fall)

for $D < 0$ applies $\lambda_{1/2} = \underbrace{-\frac{R}{2L}}_{\delta} \pm j \cdot \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}_{\omega_d} \Rightarrow 2 \text{ compl. EW}$

(3)

2.) Homogeneous solution: (fleeting)

$$u_{C,h} = e^{-\delta t} \cdot C_0 \cdot \sin(\omega_d t + \varphi_0) \quad \text{with} \quad \lambda_{1/2} = -\delta \pm j \omega_d$$

(4)

Derivation for $u_{C,h}$ in Excursus. Determination of the constants C_0 and φ_0 as known.


Periodic case for the RLC series resonant circuit

3.) Particular solution: (settled in)

$$u_{C,p} = U_q$$

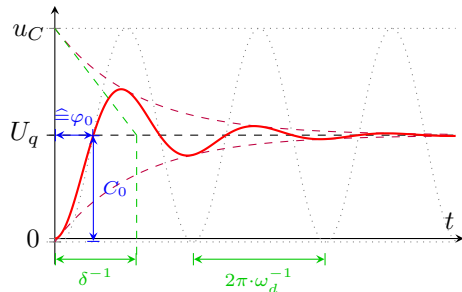4.) General solution: (Superposition)

$$u_C(t) = e^{-\delta t} \cdot C_0 \cdot \sin(\omega_d t + \varphi_0) + U_q$$



5.) Determine constants: (as known)

1. AB: $u_C(0) = e^{-\cancel{\delta 0}} \cdot C_0 \cdot \sin(\cancel{\omega_d t} + \varphi_0) + U_q \stackrel{!}{=} 0$

2. AB: $\frac{d}{dt} u_C(0) = -\delta \cdot e^{-\cancel{\delta 0}} \cdot C_0 \cdot \sin(\varphi_0) + e^{-\cancel{\delta 0}} \cdot C_0 \cdot \omega_d \cdot \cos(\varphi_0) \stackrel{!}{=} 0$

$$\Rightarrow C_0 = -\frac{U_q}{\sin(\varphi_0)} \quad \text{and} \quad \varphi_0 = \arctan\left(\frac{\omega_d}{\delta}\right)$$

Excursion: Derivation of the homogeneous solution in the periodic case

$$u_{C,h} = e^{-\delta t} \cdot (K_1 \cdot e^{+j\omega_d t} + K_2 \cdot e^{-j\omega_d t}) \quad (5)$$

K_1 and K_2 must be complex conjugates so that $u_{C,h}$ is real!

with $K_1 = a + jb$ and $K_2 = a - jb$ with $a, b \in \mathbb{R}$

$$u_{C,h} = e^{-\delta t} \cdot [(a + jb) \cdot e^{+j\omega_d t} + (a - jb) \cdot e^{-j\omega_d t}]$$

$$u_{C,h} = e^{-\delta t} \cdot \left[a \cdot \underbrace{(e^{+j\omega_d t} + e^{-j\omega_d t})}_{2 \cos(\omega_d t)} + jb \cdot \underbrace{(e^{+j\omega_d t} - e^{-j\omega_d t})}_{2j \sin(\omega_d t)} \right]$$

with $e^{+jx} + e^{-jx} = \cos(x) + \cancel{j \sin(x)} + \cos(x) - \cancel{j \sin(x)} = 2 \cos(x)$


$$e^{+jx} - e^{-jx} = \cancel{\cos(x)} + j \sin(x) - \cancel{\cos(x)} + j \sin(x) = 2j \sin(x)$$

$$u_{C,h} = e^{-\delta t} \cdot \left[\underbrace{2a}_{C_1} \cdot \cos(\omega_d t) - \underbrace{2b}_{C_2} \cdot \sin(\omega_d t) \right] \quad (6)$$

Excursion: Derivation of the homogeneous solution in the periodic case

Superposition of two oscillations with the same angular frequency ω_d :
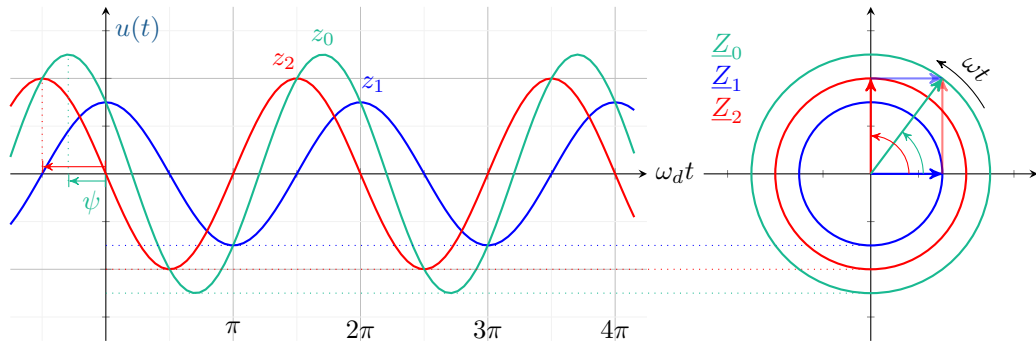
$$u_{C,h} = e^{-\delta t} \cdot \left[\underbrace{2a}_{C_1} \cdot \cos(\omega_d t) - \underbrace{2b}_{C_2} \cdot \sin(\omega_d t) \right]$$



$$u_{C,h} = e^{-\delta t} \cdot C_0 \cdot \sin(\omega_d t + \varphi_0)$$

$$\text{with } \lambda_{1/2} = -\delta \pm j \cdot \omega_d$$

Excursion: Derivation of the homogeneous solution in the periodic case

$$u_{C,h} = e^{-\delta t} \cdot \left[\underbrace{2a}_{C_1} \cdot \cos(\omega_d t) - \underbrace{2b}_{C_2} \cdot \sin(\omega_d t) \right]$$

Time domain

Polarform

Cartesian

$$z_1(t) = +C_1 \cdot \cos(\omega_d t)$$

$$\Leftrightarrow \underline{z}_1 = C_1 \cdot e^{j0}$$

$$\underline{z}_1 = C_1$$

$$z_2(t) = -C_2 \cdot \sin(\omega_d t)$$

$$\Leftrightarrow \underline{z}_2 = C_2 \cdot e^{-j\frac{\pi}{2}}$$

$$\underline{z}_2 = -j \cdot C_2$$

$$z_0(t) = z_1(t) + z_2(t)$$

$$\Leftrightarrow \underline{z}_0 = \underline{z}_1 + \underline{z}_2$$

$$\underline{z}_0 = C_1 - j \cdot C_2$$

$$= C_0 \cdot \cos(\omega_d t + \psi)$$


$$\Leftrightarrow = C_0 \cdot e^{j\psi}$$

with $C_0 = \sqrt{C_1^2 + C_2^2}$ and $\psi = \arctan\left(-\frac{C_2}{C_1}\right), \quad \varphi_0 = \psi + \frac{\pi}{2}$

$$z_0(t) = C_0 \cdot \sin(\omega_d t + \varphi_0) \tag{7}$$


$$u_{C,h} = e^{-\delta t} \cdot C_0 \cdot \sin(\omega_d t + \varphi_0) \quad \text{with} \quad \lambda_{1/2} = -\delta \pm j \cdot \omega_d$$

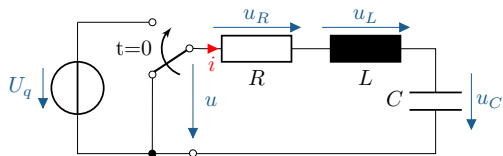Excursion: Digression: Case differentiation for RLC series resonant circuits, zero points



$$\lambda_{1/2} = -\frac{R}{2L} \pm \sqrt{\underbrace{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}_{\text{Discriminant } D}}$$

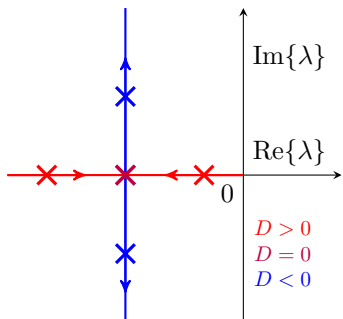Zero points in the locus diagram: $\lambda(D)$ for $\delta = \frac{R}{2L} = \text{const.}$




$\text{Re}\{\lambda\} < 0: \Rightarrow \text{stable}$

$D > 0$: NST closer to the Im-axis
 $\Rightarrow$ slower, dominant

$D = 0$: NST further away from the Im-axis
 $\Rightarrow$ fastest aperiodic case

$D < 0$: NST conjugated, complex
 $\Rightarrow$ oscillating

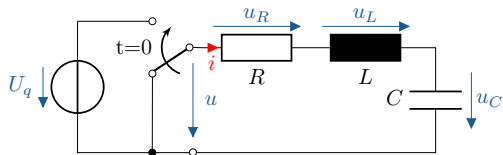Digression: Decay constant, natural and resonance circuit frequency, quality factor



$$\lambda_{1/2} = - \underbrace{\frac{R}{2L}}_{\delta} \pm j \cdot \underbrace{\sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}}_{\omega_d}$$

Periodic case: Relationship between δ , ω_d , ω_0 and Q_S :

Resonant circuit frequency: $\omega_0 = \sqrt{\frac{1}{LC}}$ with $\text{Im}\{\underline{Z}(\omega_0)\} \stackrel{!}{=} 0$

Damped natural frequency: $\omega_d = \sqrt{\omega_0^2 - \delta^2}$ Undamped equal ω_0

Quality factor: $Q_S = \frac{X_{L,0}}{R} = \frac{\omega_0 L}{R} = \frac{\omega_0}{2\delta}$ Measure of vibration capability

Comparison of homo. ODEs: $0 = \ddot{y} + 2\delta \cdot \dot{y} + \omega_0^2 \cdot y$ linearly damped oscillation